

數位邏輯設計 Ch9 HW

注意事項：請寫出詳細計算與分析過程，不可以只寫答案!

Problems:

- 9.2** Figure 9.111 shows a mod-16 which controls the operation of two digital sequential circuits, labeled Circuit 1 and Circuit 2. Circuit 1 is positive edge-triggered and clocked by counter output Q_1 . Circuit 2 is negative edge-triggered and clocked by Q_3 . (Q_3 is the MSB output of the counter.)

 


FIGURE 9.111 Problem 9.2: Mod-16 Counter Driving Two Sequential Circuits

- Draw the timing diagram for one complete cycle of the circuit operation. Draw arrows on the active edges of the waveforms that activate Circuit 1 and Circuit 2.
 - State how many times Circuit 1 is clocked for each time that Circuit 2 is clocked.
- 9.11** Draw the circuit for a synchronous mod-16 UP counter made from negative edge-triggered JK flip-flops.
- 9.55** Complete the logic circuit shown in Figure 9.117 to make a parallel-in-serial-out shift register.

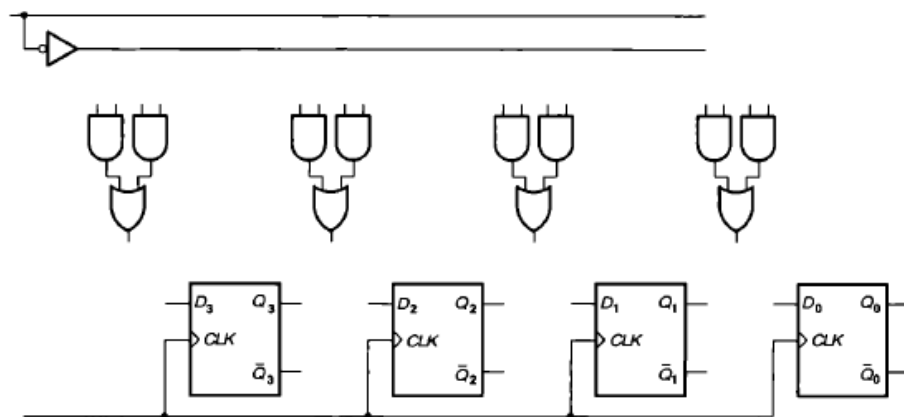


FIGURE 9.117 Problem 9.55: Logic Circuit