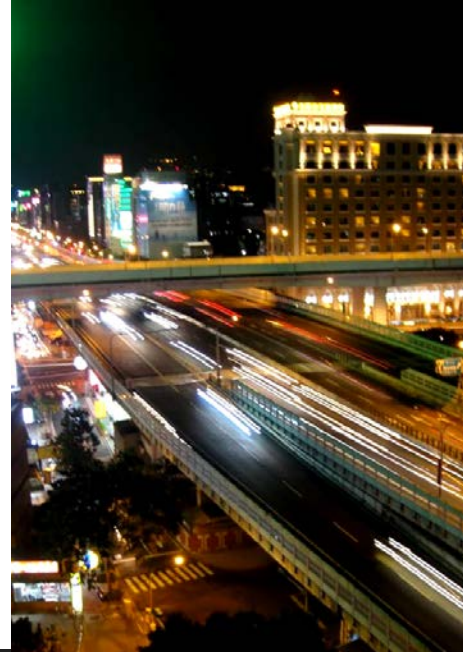




國立臺北科技大學



# 電路學 Circuit Theory

## Lecture 3

# Responses of RL, RC, and RLC Circuits

Week 9, Fall 2019

陳晏笙

*Electronic Engineering, Taipei Tech*



# Contents

## Lecture 3:

### Responses of RL, RC, and RLC Circuits

- 3.1 Capacitors and Inductors
- 3.2 Combinations of C and L
- 3.3 Natural Responses of First-Order Circuits
- 3.4 Step Responses of First-Order Circuits
- 3.5 Linear Second-Order Circuits
- 3.6 Responses of Second-Order Circuits







# Contents



## 3.1 Capacitors and Inductors




# Two New Passive Components: C & L

## Resistors:

- They dissipate energy

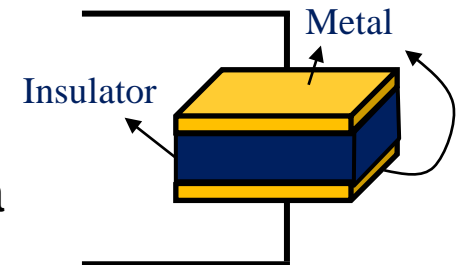
## Capacitors:

- They store energy
- The energy is stored at electric field
- Whenever electrical conductors are separated by a insulator, the capacitance occurs




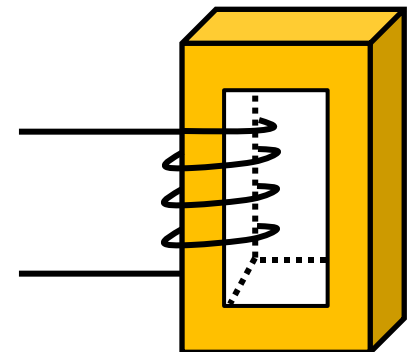
## Inductors

- They store energy
- The energy is stored at magnetic field
- Inductance results from a conductor linking a magnetic field





# Component Model of a Capacitor

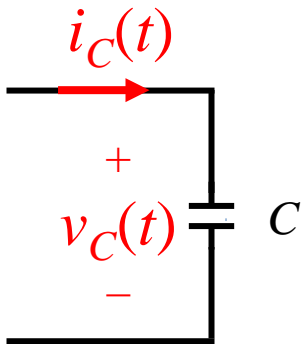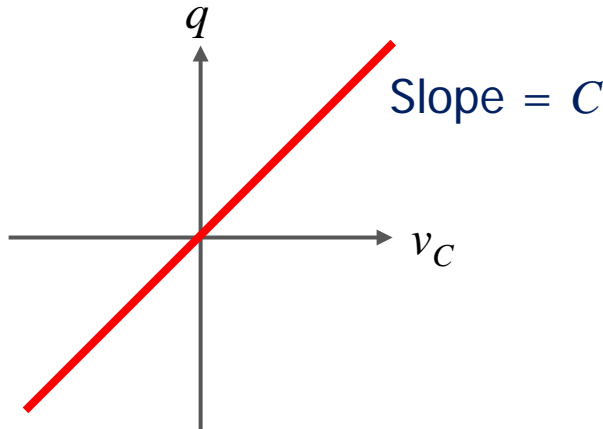Symbol	Model
	

■  $q = C \times v_C$ ; where  $q$ : charge, or “electric flux”, in coulombs  
 $C$ : capacitance in F (Farad)


■ On the other hand,  $q(t) = \int_{-\infty}^t i_C(\tau) d\tau$

1. If  $v_C$  is given, then  $i_C(t) = \frac{dq}{dt} = C \frac{dv_C(t)}{dt}$


2. If  $i_C$  is given, then  $v_C(t) = \frac{q}{C} = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau = v_C(t_0) + \frac{1}{C} \int_{t_0}^t i_C(\tau) d\tau$

## EX 3.1
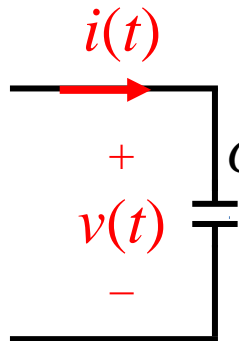
## Circuit Variables of a Capacitor (1/5)


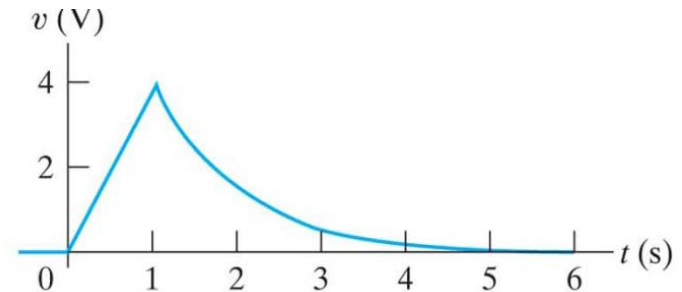
$$v(t) = \begin{cases} 0 & t \leq 0 \text{ s} \\ 4t \text{ V} & 0 < t \leq 1 \text{ s} \\ 4e^{-(t-1)} \text{ V} & t > 1 \text{ s} \end{cases}$$




1. Find the expressions for the current, power, and energy on the capacitor
2. Determine the interval of time when energy is being stored and delivered in the capacitor, respectively

## EX 3.1
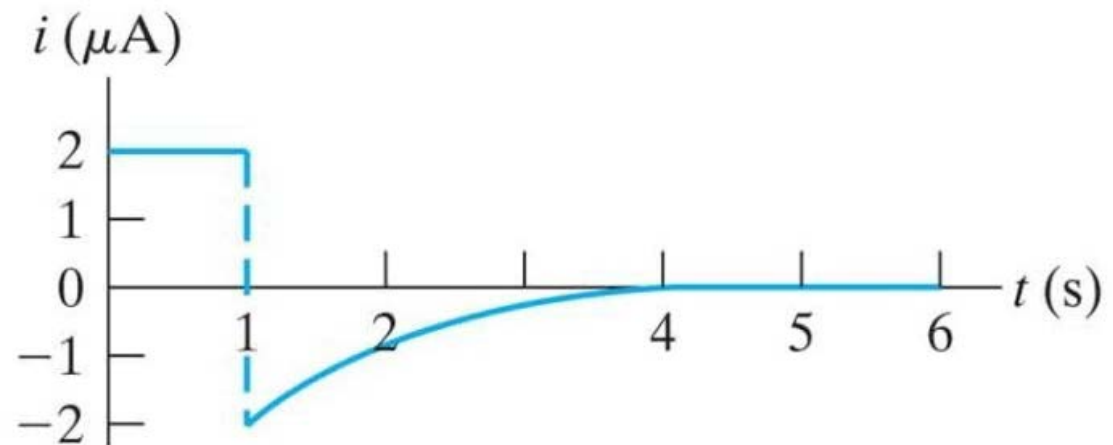
## Circuit Variables of a Capacitor (2/5)

📖 The current run through the capacitor:  $i(t) = C \frac{dv(t)}{dt}$

$$\rightarrow i(t) = \begin{cases} & t \leq 0 \text{ s} \\ & 0 < t \leq 1 \text{ s} \\ & t > 1 \text{ s} \end{cases}$$




## EX 3.1
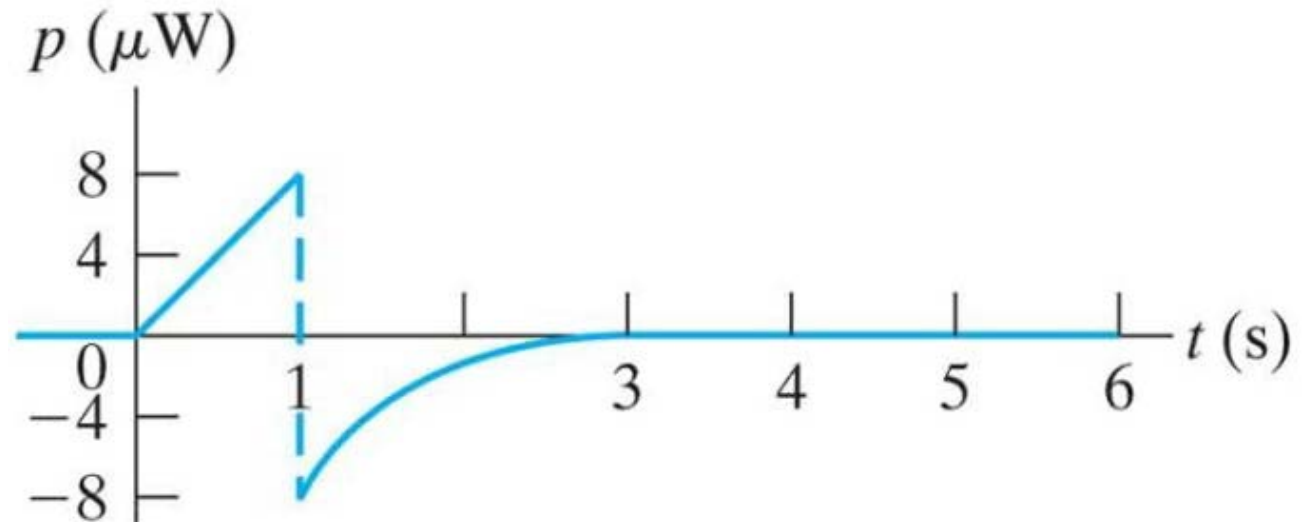
# Circuit Variables of a Capacitor (3/5)

📖 The power of the capacitor:  $p(t) = v(t)i(t)$

$$\rightarrow p(t) = \begin{cases} & t \leq 0 \text{ s} \\ & 0 < t \leq 1 \text{ s} \\ & t > 1 \text{ s} \end{cases}$$






## EX 3.1
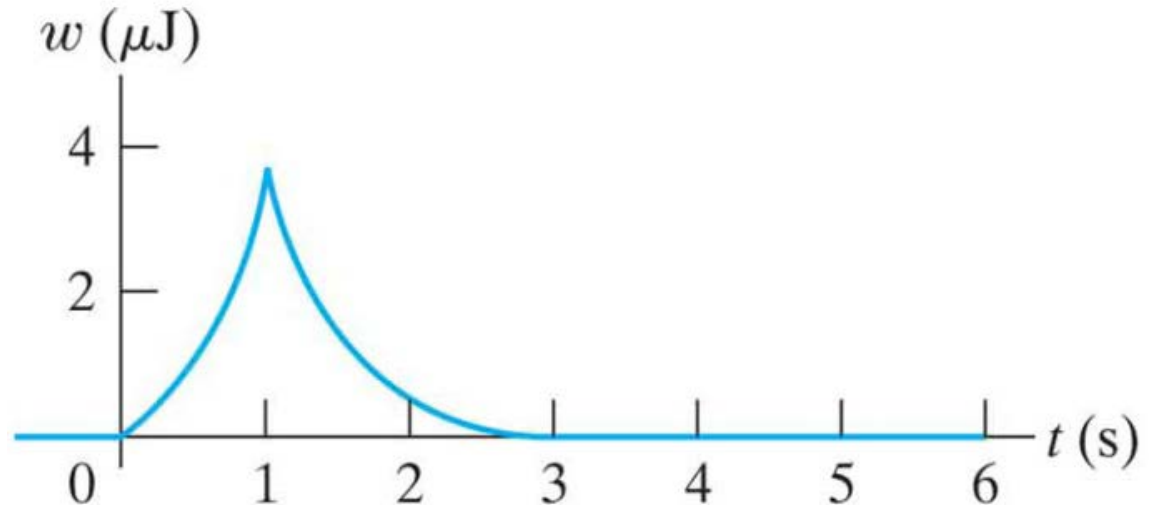
# Circuit Variables of a Capacitor (4/5)

📖 The energy of the capacitor:  $W(t) = \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t C v(\tau) \frac{dv(\tau)}{d\tau} d\tau = \frac{1}{2} C v^2(t)$




$$W(t) = \begin{cases} & t \leq 0 \text{ s} \\ & 0 < t \leq 1 \text{ s} \\ & t > 1 \text{ s} \end{cases}$$



# EX 3.1

# Circuit Variables of a Capacitor (5/5)

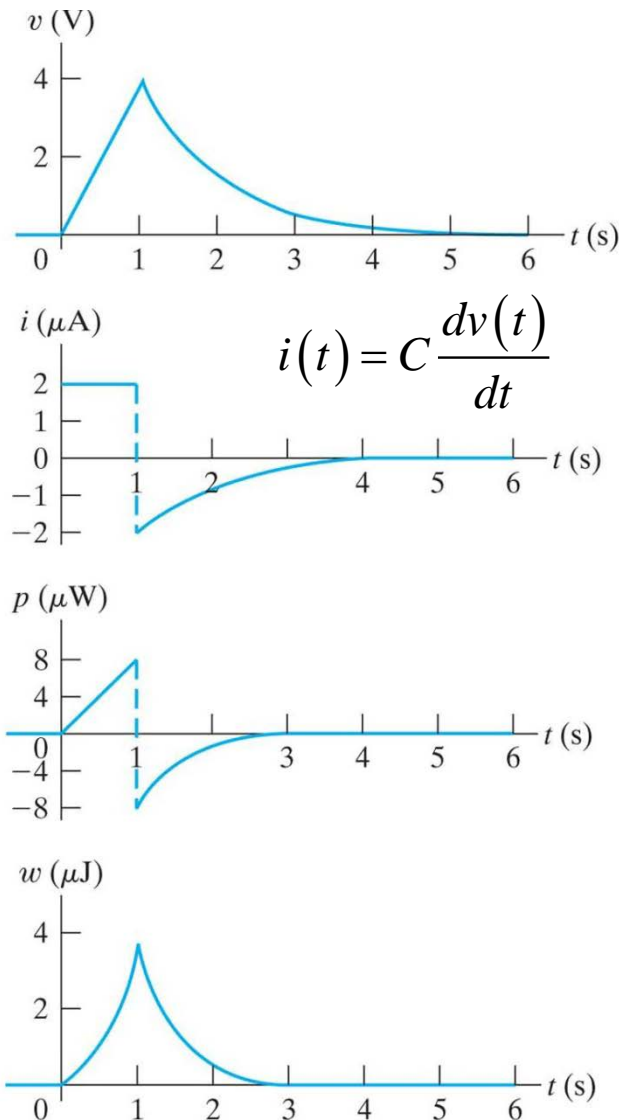

## Summary:

- Voltage on a capacitor must be continuous; it cannot change abruptly across the terminals of the capacitor
- If the voltage across the terminals is constant,  $i_c = 0$  (equivalent to open circuit)

## When does the capacitor store energy?


- Storing energy:  $w(t)$  increases
- This is when the power is positive

$$\int_0^1 p(t) dt = \int_0^1 (8t) dt = 4 \text{ } \mu\text{J}$$
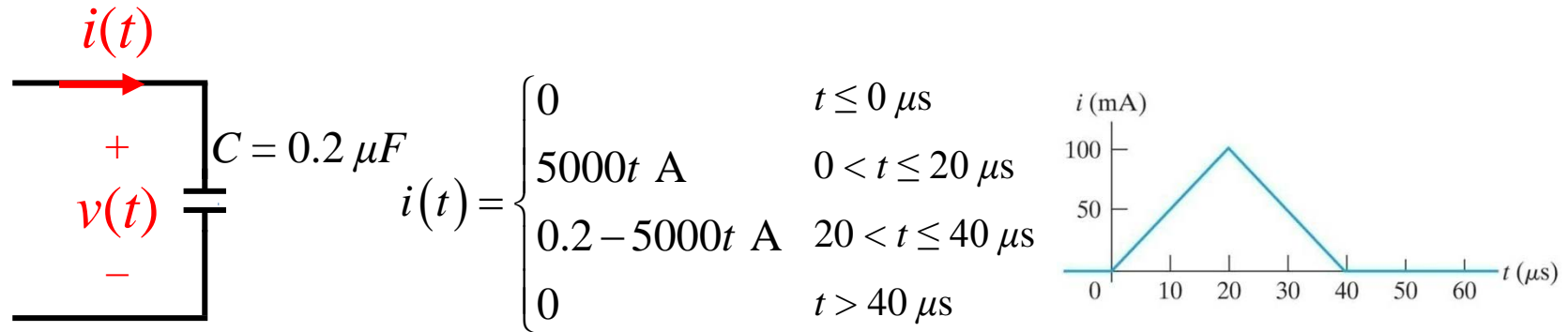
## When does the capacitor dissipate energy?

- Dissipating energy:  $w(t)$  decreases
- This is when the power is negative

$$\int_1^{\infty} p(t) dt = \int_1^{\infty} (-8e^{-2(t-1)}) dt = -4 \text{ } \mu\text{J}$$




1. Let  $v(0) = 0$ . Find the expressions for the voltage, power, and energy on the capacitor

## EX 3.2
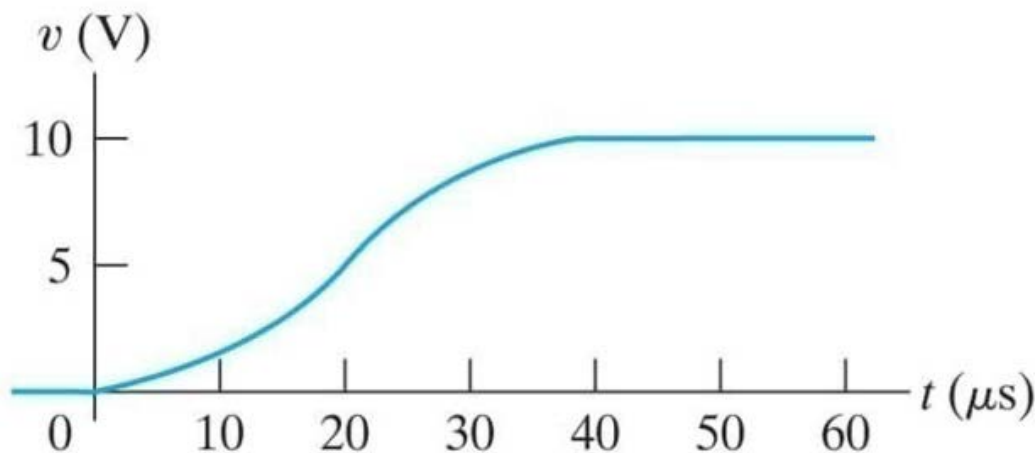
## Circuit Variables of a Capacitor (2/4)

📖 The voltage dropped across the capacitor:  $v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$


$$\rightarrow v(t) = \begin{cases} 0 & t \leq 0 \mu\text{s} \\ & 0 < t \leq 20 \mu\text{s} \\ & 20 < t \leq 40 \mu\text{s} \\ & t > 40 \mu\text{s} \end{cases}$$





❏ The power in the capacitor:  $p(t) = v(t)i(t)$
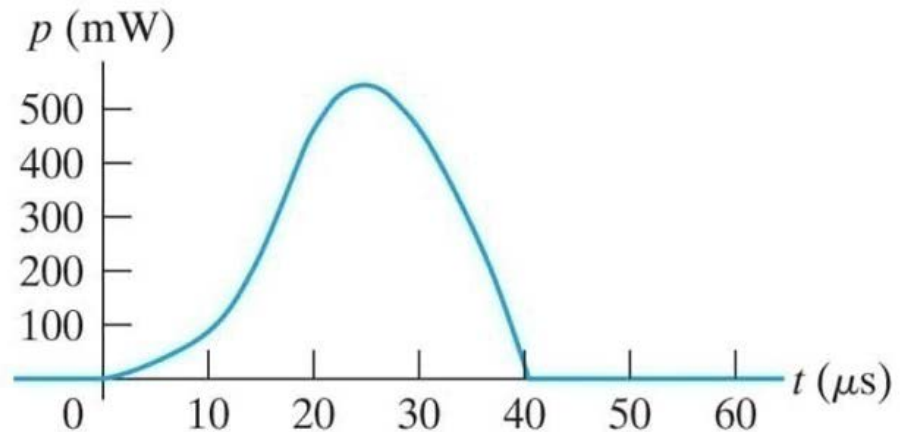
$$\rightarrow p(t) = \begin{cases} 0 & t \leq 0 \mu s \\ (12.5 \times 10^9 t^2) \times (5000t) = 62.5 \times 10^{12} t^3 \text{ W} & 0 < t \leq 20 \mu s \\ (10^6 t - 12.5 \times 10^9 t^2 - 10) \times (0.2 - 5000t) = 62.5 \times 10^{12} t^3 - 7.5 \times 10^9 t^2 + 2.5 \times 10^5 t - 2 \text{ W} & 20 < t \leq 40 \mu s \\ 0 & t > 40 \mu s \end{cases}$$



❏ The power  $> 0$  all the time





❏ So the capacitor stores energy continuously

## EX 3.2
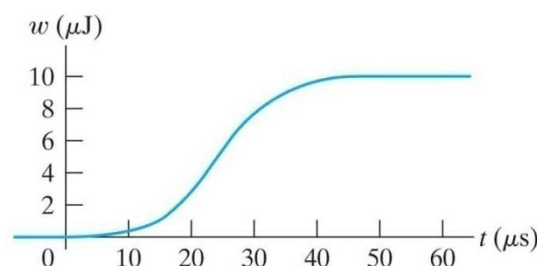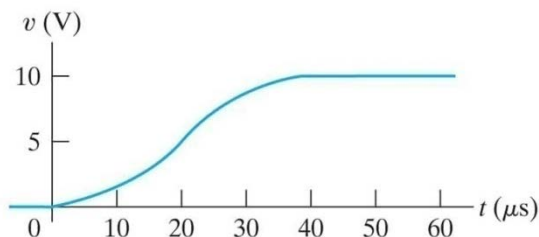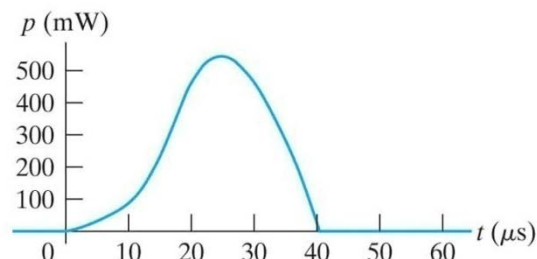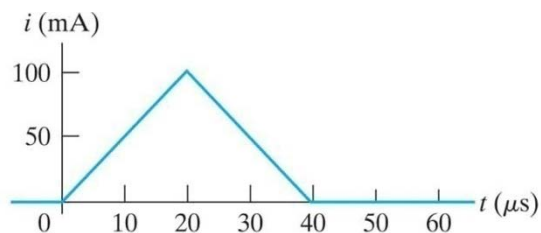
# Circuit Variables of a Capacitor (4/4)



The energy in the capacitor:  $W(t) = \frac{1}{2} C v^2(t)$

$$W(t) = \begin{cases} 0 & t \leq 0 \mu s \\ \frac{1}{2} (0.2 \times 10^{-6}) \times (12.5 \times 10^9 t^2)^2 = 15.625 \times 10^{12} t^4 J & 0 < t \leq 20 \mu s \\ \frac{1}{2} (0.2 \times 10^{-6}) \times (10^6 t - 12.5 \times 10^9 t^2 - 10)^2 = 15.625 \times 10^{12} t^4 - 2.5 \times 10^9 t^3 + 0.125 \times 10^6 t^2 - 2t + 10^{-5} J & 20 < t \leq 40 \mu s \\ \frac{1}{2} (0.2 \times 10^{-6}) \times (10)^2 = 10 \mu J & t > 40 \mu s \end{cases}$$





# Component Model of an Inductor

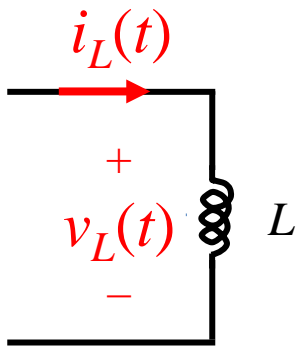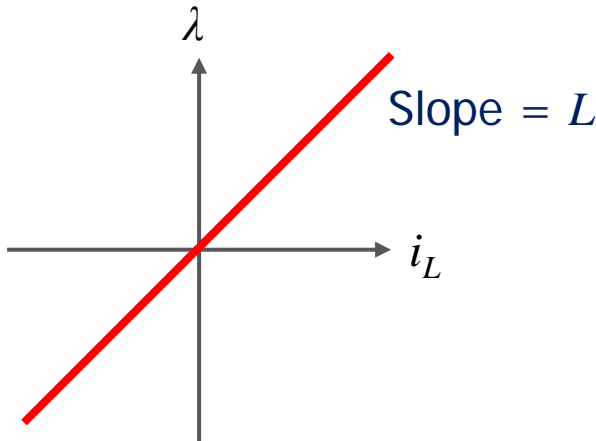Symbol	Model
	

■  $\lambda = L \times i_L$ ;      where     $\lambda$ : “magnetic flux” in weber  
    $L$ : inductance in H (Henry)


■ On the other hand,  $\lambda(t) = \int_{-\infty}^t v_L(\tau) d\tau$

1. If  $i_L$  is given, then  $v_L(t) = \frac{d\lambda}{dt} = L \frac{di_L(t)}{dt}$


2. If  $v_L$  is given, then  $i_L(t) = \frac{\lambda}{L} = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau = i_L(t_0) + \frac{1}{L} \int_{t_0}^t v_L(\tau) d\tau$

## EX 3.3

# Circuit Variables of an Inductor (1/5)

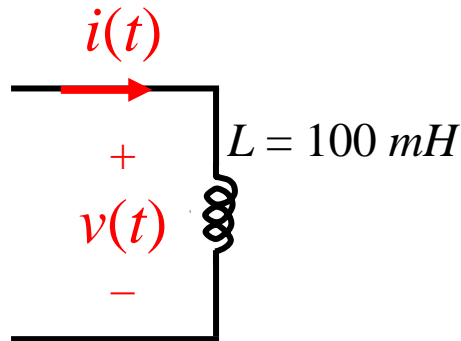
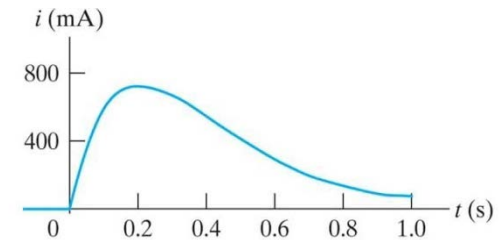
$$i(t) = \begin{cases} 0 & t \leq 0 \text{ s} \\ 10te^{-5t} \text{ A} & t > 0 \text{ s} \end{cases}$$



1. Find the expressions for the voltage, power, and energy on the inductor
2. Determine the interval of time when energy is being stored and delivered in the inductor, respectively




## EX 3.3
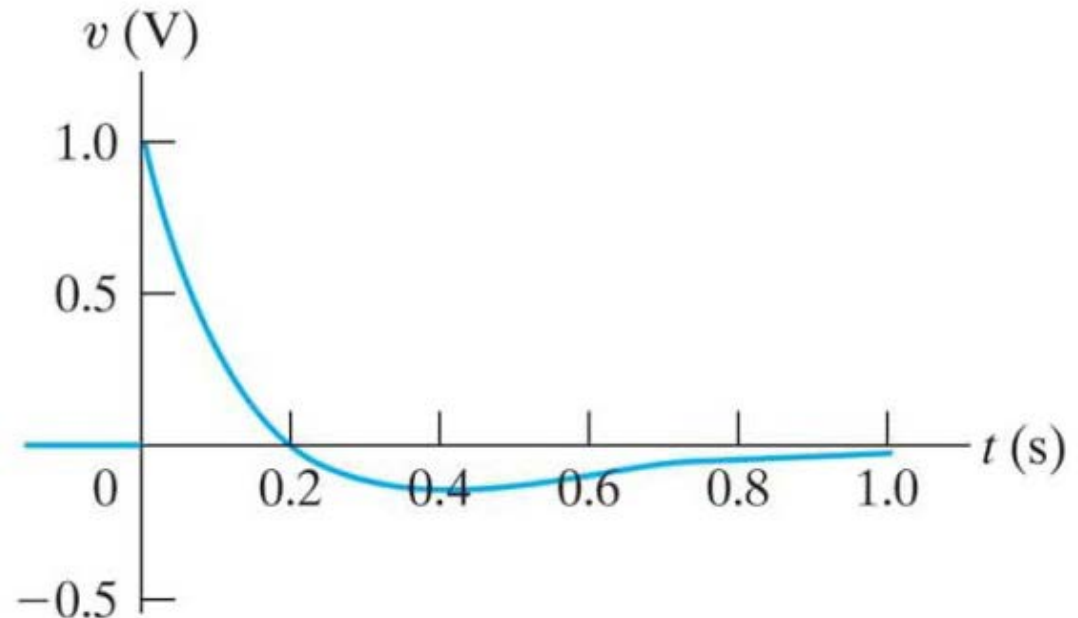
## Circuit Variables of an Inductor (2/5)

📖 The voltage dropped on the inductor:  $v(t) = L \frac{di(t)}{dt}$

➡ 
$$v(t) = \begin{cases} & t \leq 0 \text{ s} \\ & t > 0 \text{ s} \end{cases}$$




## EX 3.3
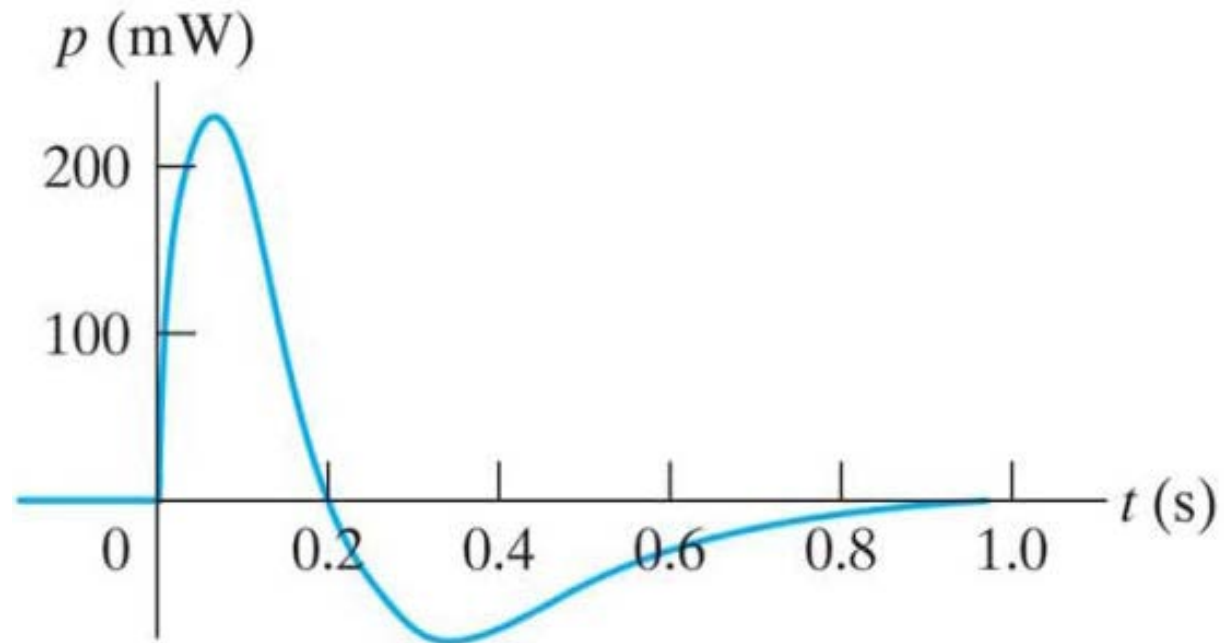
# Circuit Variables of an Inductor (3/5)

📖 The power in the inductor:  $p(t) = v(t)i(t)$

$$\rightarrow p(t) = \begin{cases} & t \leq 0 \text{ s} \\ & t > 0 \text{ s} \end{cases}$$




## EX 3.3
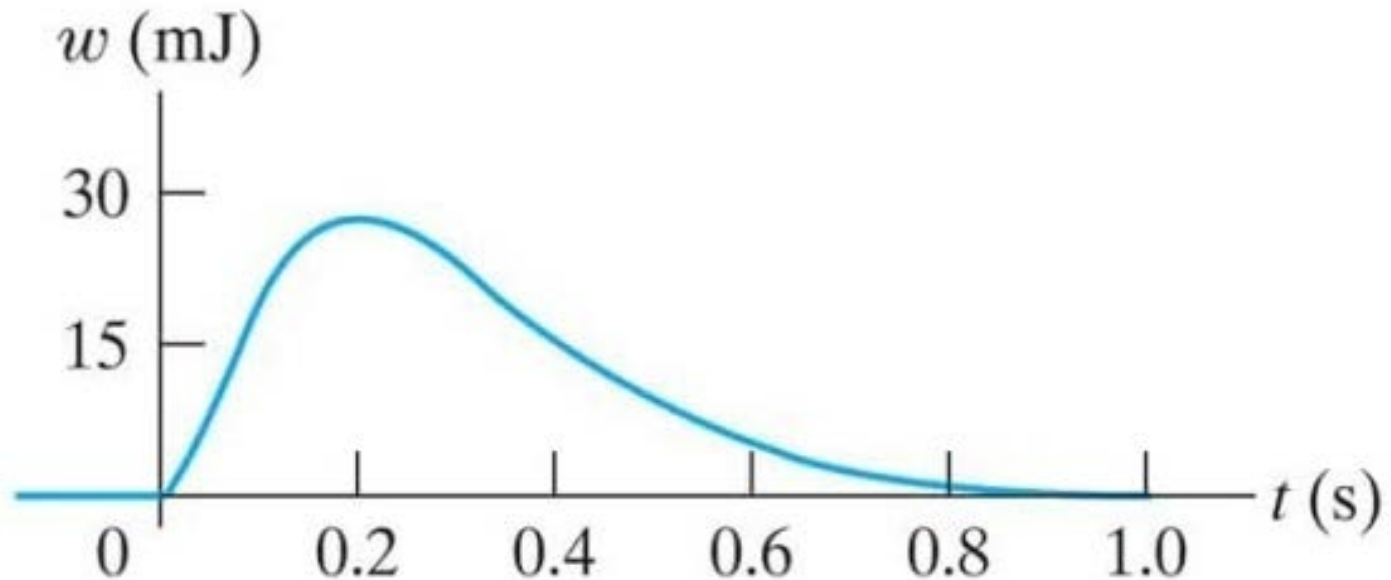
# Circuit Variables of an Inductor (4/5)


📖 The energy in the inductor:  $W(t) = \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t Li(\tau) \frac{di(\tau)}{d\tau} d\tau = \frac{1}{2} Li^2(t)$

$$\rightarrow W(t) = \begin{cases} & t \leq 0 \text{ s} \\ & t > 0 \text{ s} \end{cases}$$



## EX 3.3

# Circuit Variables of an Inductor (5/5)

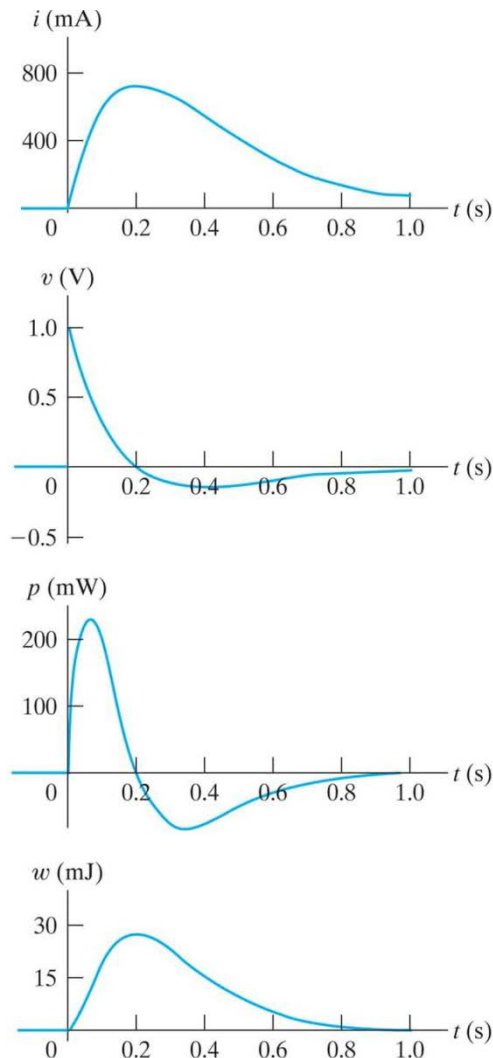

### Summary:

- Current through an inductor must be continuous; it cannot change abruptly in an inductor
- If the current run through an inductor is constant,  $v_L = 0$  (equivalent to short circuit)

### When does the inductor store energy?

- Storing energy:  $w(t)$  increases
- This is when the power is positive


$$\int_0^{0.2} p(t) dt = 27.07 \text{ mJ}$$
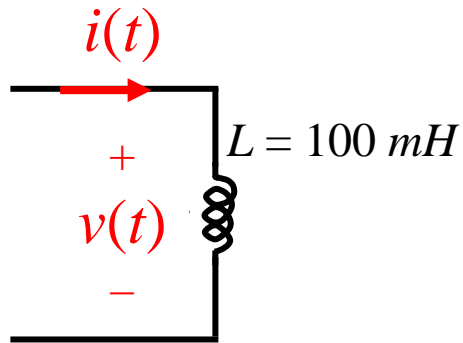
### When does the inductor dissipate energy?

- Dissipating energy:  $w(t)$  decreases
- This is when the power is negative


$$\int_{0.2}^{\infty} p(t) dt = -27.07 \text{ mJ}$$





$$v(t) = 20te^{-10t} \text{ V} \quad t > 0 \text{ s}$$

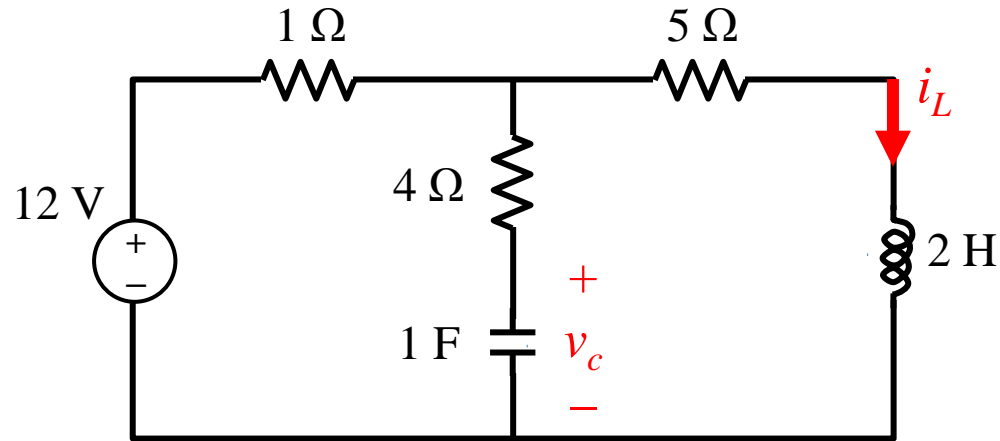1. Let  $i(0) = 0$ . Find the expressions for the current through the inductor



Under DC condition, find:

1. the voltage across the capacitor
2. the current through the inductor
3. the energy in the capacitor
4. the energy in the inductor



# Remarks

- 📖 C and L are capable of storing energy, so they can be used for generating a large amount of voltage or current for a short period of time
- 📖 They can also be used as temporary voltage or current sources
- 📖 The frequency sensitive property of L and C makes them useful for frequency discrimination
  - Low pass filters
  - High pass filters
  - Band pass filters



# Contents




## 3.2 Combinations of C and L





# N Capacitors in Parallel

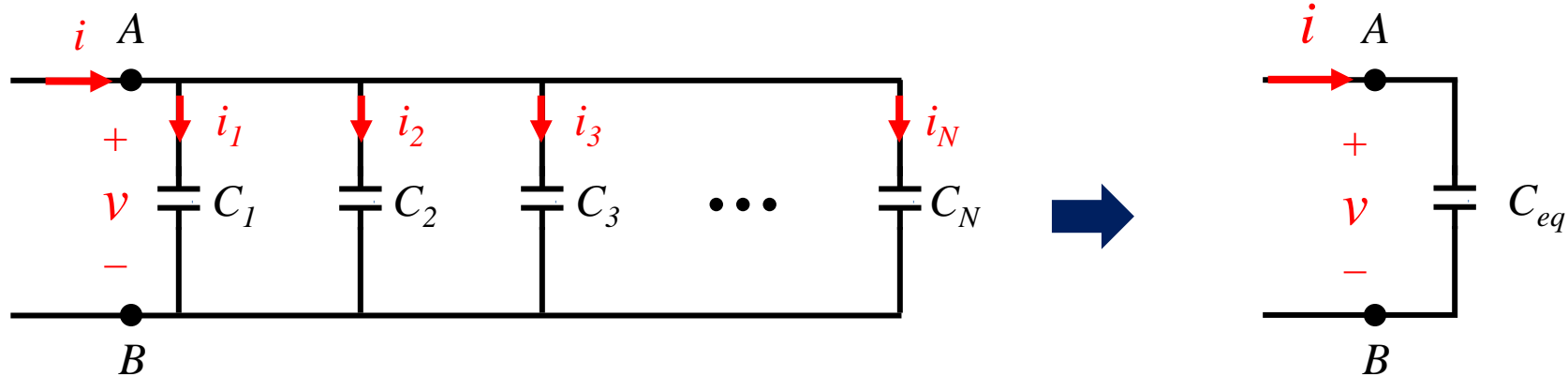

Left:  $i = i_1 + i_2 + i_3 + \dots + i_N$

$$= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$
$$= (C_1 + C_2 + C_3 + \dots + C_N) \frac{dv}{dt}$$


Right:  $i = C_{eq} \frac{dv}{dt}$



$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$



# N Capacitors in Series

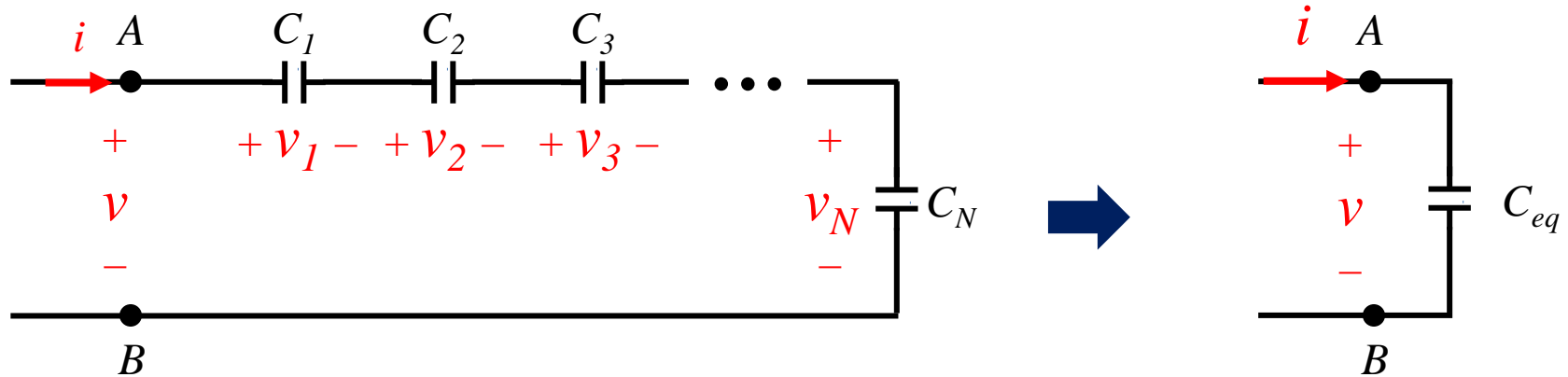

Left:  $v = v_1 + v_2 + v_3 + \dots + v_N$

$$\begin{aligned} &= \left[ v_1(t_0) + \frac{1}{C_1} \int_{t_0}^t i(\tau) d\tau \right] + \left[ v_2(t_0) + \frac{1}{C_2} \int_{t_0}^t i(\tau) d\tau \right] + \dots + \left[ v_N(t_0) + \frac{1}{C_N} \int_{t_0}^t i(\tau) d\tau \right] \\ &= (v_1(t_0) + v_2(t_0) + \dots + v_N(t_0)) + \left( \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i(\tau) d\tau \end{aligned}$$


Right:  $v = v(t_0) + \frac{1}{C_{eq}} \int_{t_0}^t i(\tau) d\tau$



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$



# N Inductors in Series

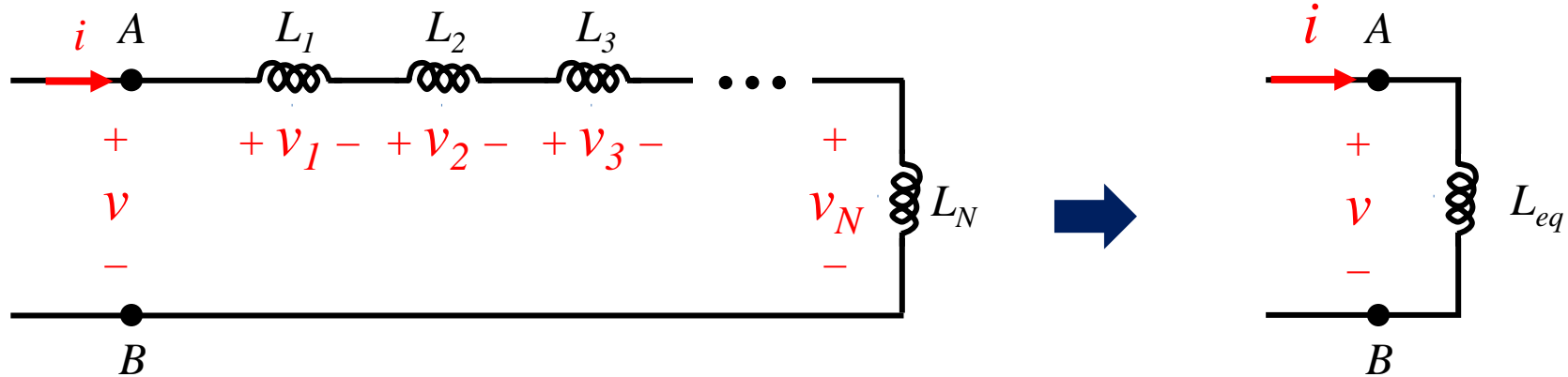

Left:  $v = v_1 + v_2 + v_3 + \dots + v_N$

$$\begin{aligned} &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \dots + L_N \frac{di}{dt} \\ &= (L_1 + L_2 + L_3 + \dots + L_N) \frac{di}{dt} \end{aligned}$$


Right:  $v = L_{eq} \frac{di}{dt}$



$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$



# N Capacitors in Parallel

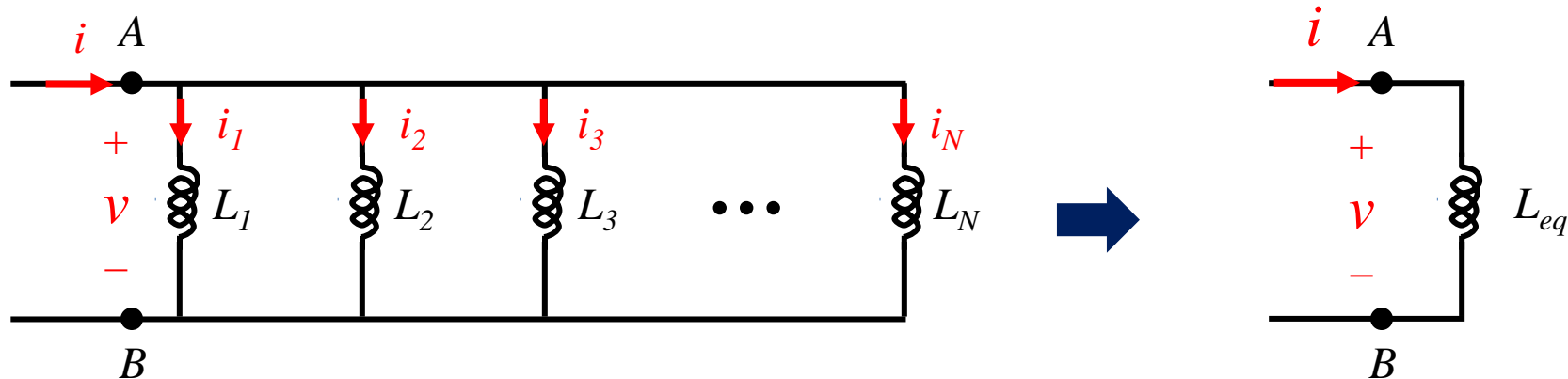

Left:  $i = i_1 + i_2 + i_3 + \dots + i_N$

$$\begin{aligned} &= \left[ i_1(t_0) + \frac{1}{L_1} \int_{t_0}^t v(\tau) d\tau \right] + \left[ i_2(t_0) + \frac{1}{L_2} \int_{t_0}^t v(\tau) d\tau \right] + \dots + \left[ i_N(t_0) + \frac{1}{L_N} \int_{t_0}^t v(\tau) d\tau \right] \\ &= (i_1(t_0) + i_2(t_0) + \dots + i_N(t_0)) + \left( \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int_{t_0}^t v(\tau) d\tau \end{aligned}$$

Right:  $i = i(t_0) + \frac{1}{L_{eq}} \int_{t_0}^t v(\tau) d\tau$



$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$



# Summary

	Resistor	Capacitor	Inductor
Give $i$ , find $v$	$v = iR$	$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$	$v = L \frac{di}{dt}$
Give $v$ , find $i$	$i = \frac{v}{R}$	$i = C \frac{dv}{dt}$	$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$
Power or energy	$P = i^2 R = \frac{v^2}{R}$	$W = \frac{1}{2} C v^2$	$W = \frac{1}{2} L i^2$
Series connection	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel connection	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
DC case	<b>The same</b>	<b>Open circuit</b>	<b>Short circuit</b>



# Contents



## **3.3 Natural Responses of First-Order Circuits**



# From Resistive Circuits to RC and RL Circuits

## Resistive circuits

- Algebraic equations
- Solution techniques:  
Nodal analysis  
Mesh analysis

## RC and RL circuits

- Differential equations
- Solution techniques:  
Nodal analysis  
Mesh analysis

When input sources are set as DC inputs, the “forced response” is called a “step response”


- The solution of RC and RL circuits:  
**Natural response + Forced response**
- Or in the form of  
**Transient response + Steady response**
- Or in the mathematical terms of  
**Homogeneous solution + Particular solution**






# Natural Responses of First-Order Circuits

## First-order RC circuit

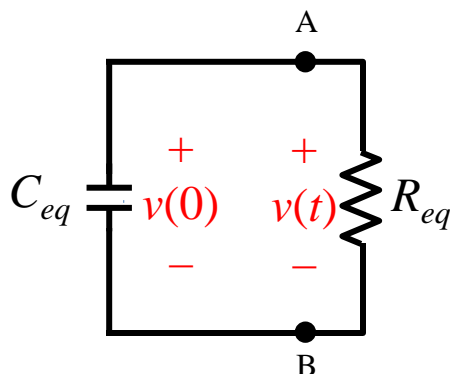


Objective: Find  $v(t)$  from a given  $v(0)$

How to create  $v(0)$ ?

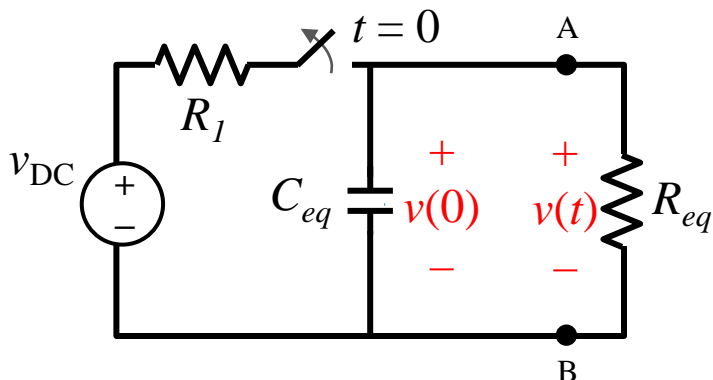


## First-order RL circuit

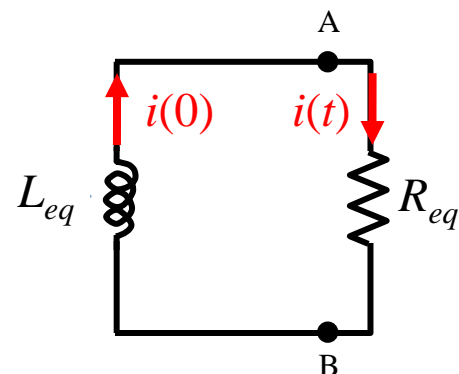





Objective: Find  $i(t)$  from a given  $i(0)$

How to create  $i(0)$ ?

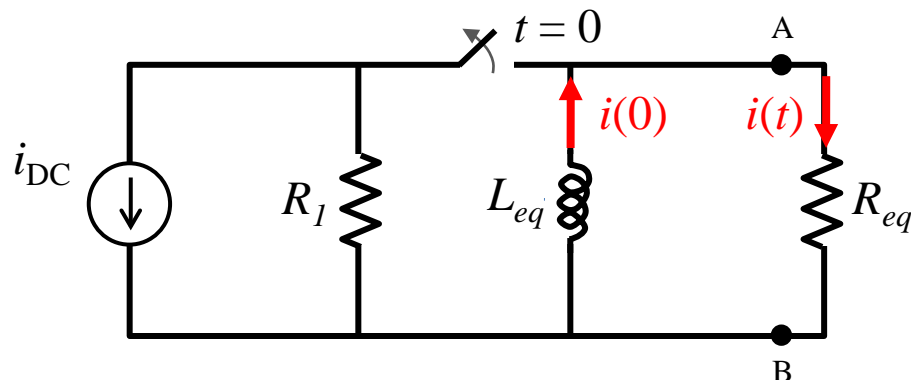




# Step Responses of First-Order Circuits

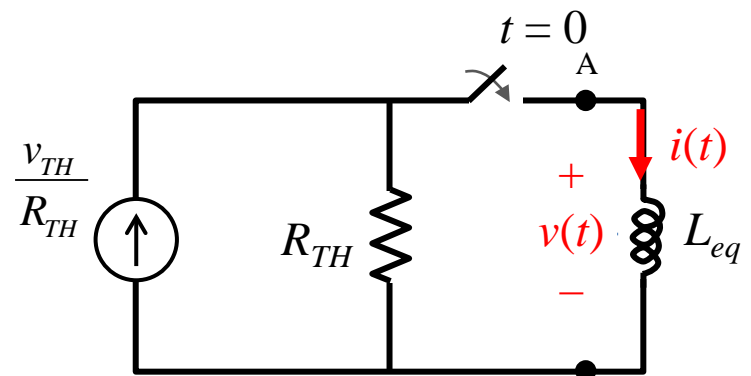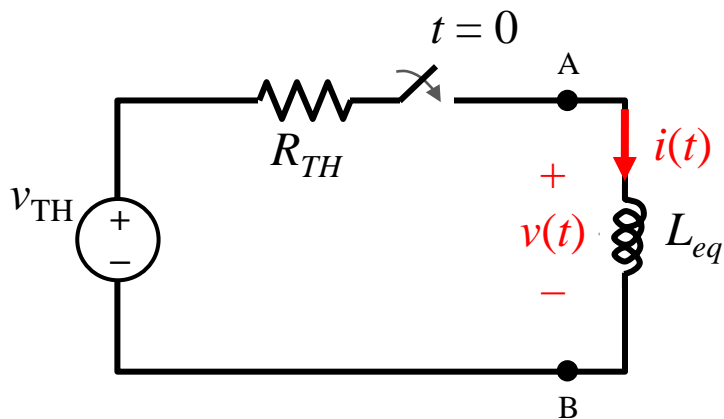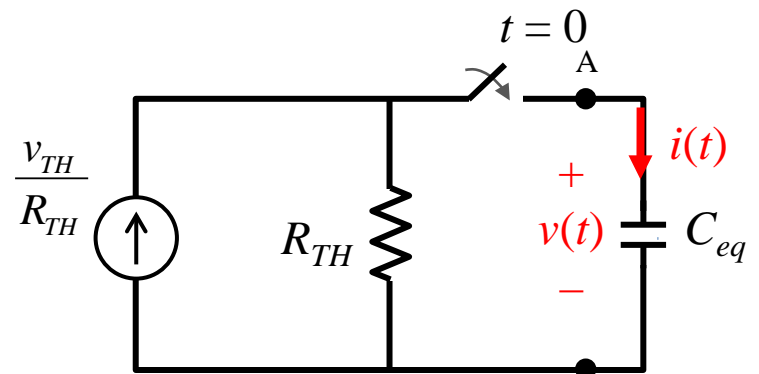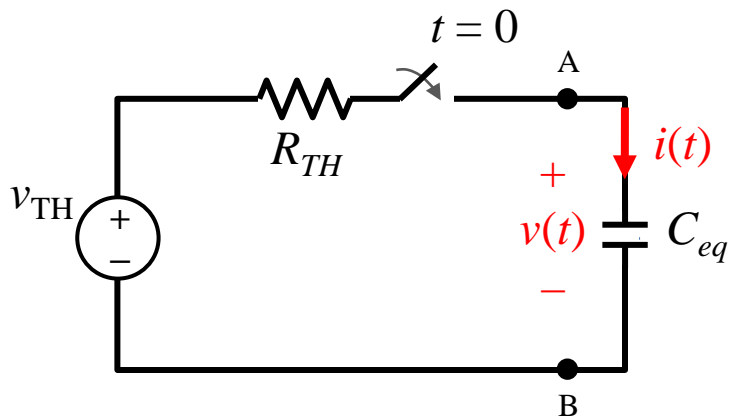

- Objective: Find  $v(t)$  and  $i(t)$  after  $t = 0$
- Note that the voltage source and current source provide DC inputs

## EX 3.6


## An RC Circuit

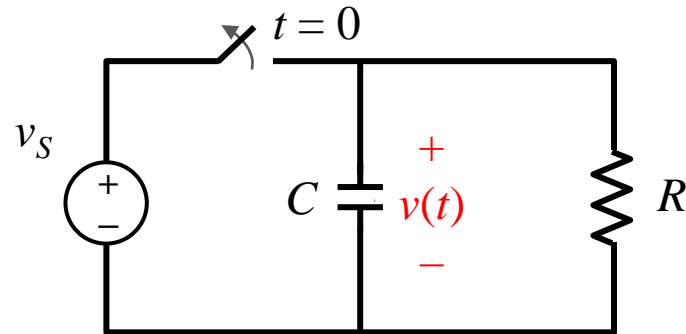

1. Find  $v(t)$  for  $t \geq 0^+$



# Time Constant in RC Circuits

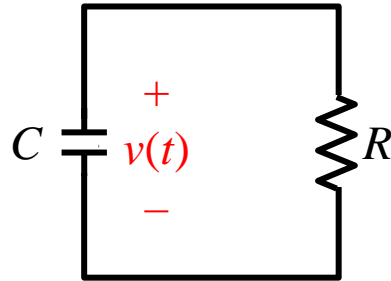


$$v(t) = v_s e^{-\frac{t}{RC}}$$

After finishing the computation, we find an interesting parameter


$$\tau = RC \longrightarrow v(t) = v_s e^{-\frac{t}{\tau}}$$

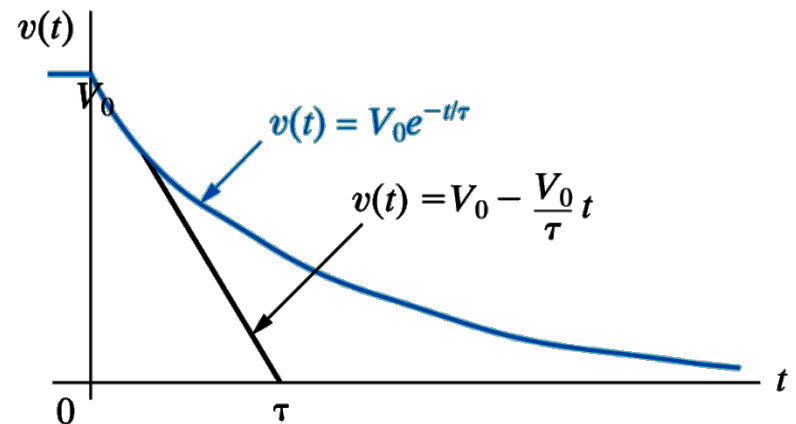- ①  $t = \tau$ :  $v(t) = 0.368 v_s$  (37 %)
- ②  $t = 3\tau$ :  $v(t) = 0.050 v_s$  (5 %)
- ③  $t = 5\tau$ :  $v(t) = 0.007 v_s \approx 0$  (1 %)



- When  $t \geq 5\tau$ , we call it a “steady state”
- The capacitor is fully discharged after  $5\tau$


## Example: Another RC Circuit

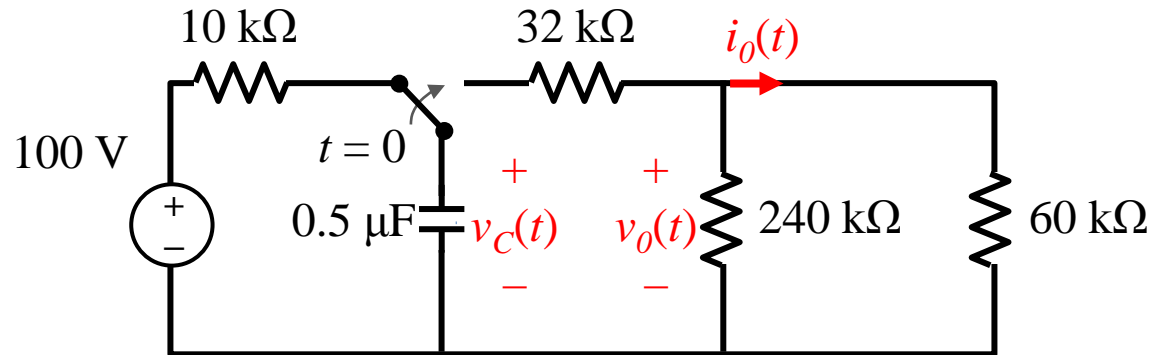

1. Find  $v_C(t)$ ,  $v_O(t)$ , and  $i_O(t)$  for  $t \geq 0^+$
2. Find the total energy dissipated in the 60-kΩ resistor

## EX 3.8


## An RL Circuit

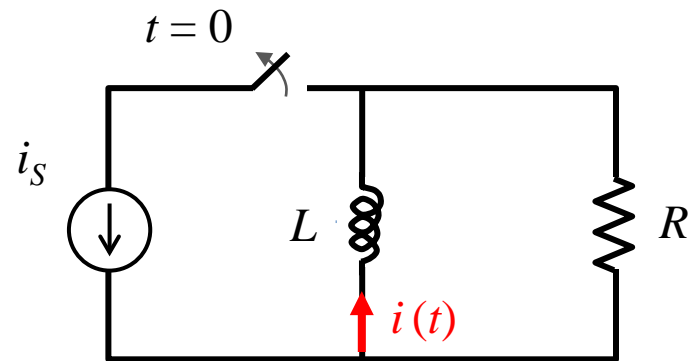

1. Find  $i(t)$  for  $t \geq 0^+$



# Time Constant in RL Circuits

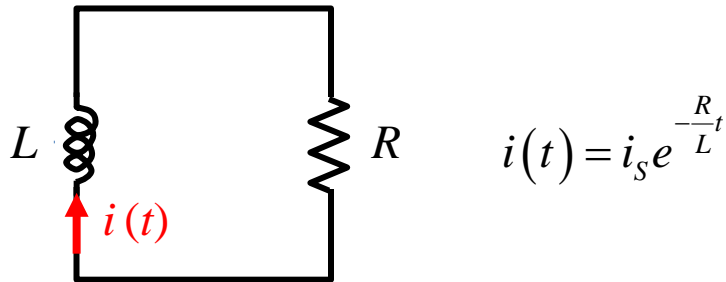


$$i(t) = i_s e^{-\frac{R}{L}t}$$

📖 In the above procedure, we find an interesting parameter again


$$\tau = \frac{R}{L} \longrightarrow i(t) = i_s e^{-\frac{t}{\tau}}$$

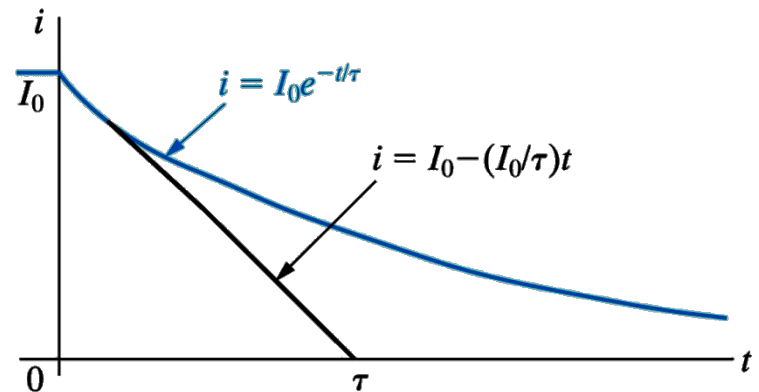- ①  $t = \tau: i(t) = 0.368 i_s$  (37 %)
- ②  $t = 3\tau: i(t) = 0.050 i_s$  (5 %)
- ③  $t = 5\tau: i(t) = 0.007 i_s \approx 0$  (1 %)




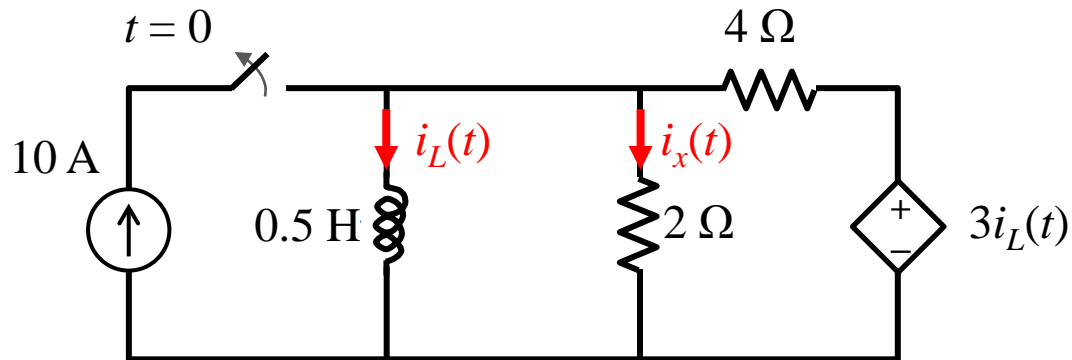- 📖 When  $t \geq 5\tau$ , we call it a “steady state”
- 📖 The inductor is fully discharged after  $5\tau$





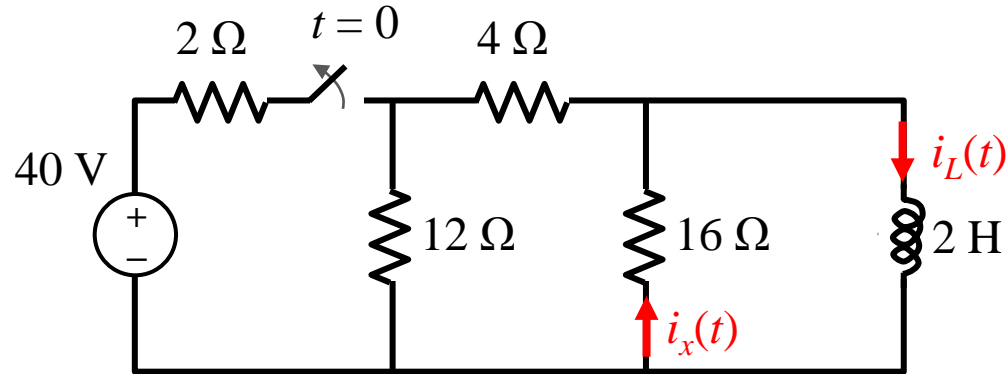1. Find  $i_L(t)$  and  $i_x(t)$  for  $t \geq 0^+$



■ The switch has been turned on for a long time

■ At  $t = 0$ , it's turned off

1. Find  $i_x(t)$  for  $t \geq 0^+$

2. Find  $i_L(t)$  for  $t \geq 0^+$



# Contents




## **3.4 Step Responses of First-Order Circuits**



# Characteristics of Step Response

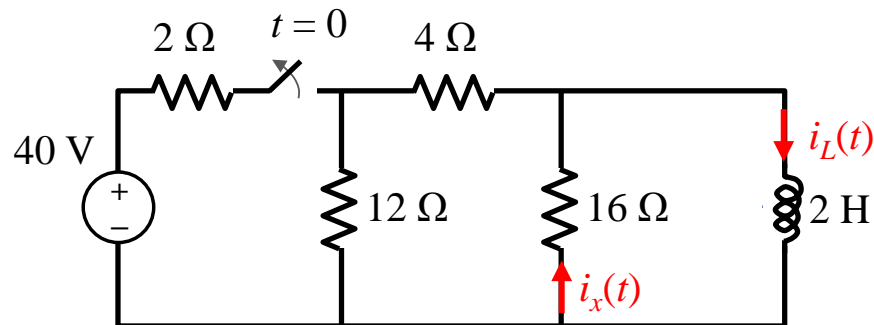
## Natural response:


- When the state of the switch is changed, the new state has no other sources


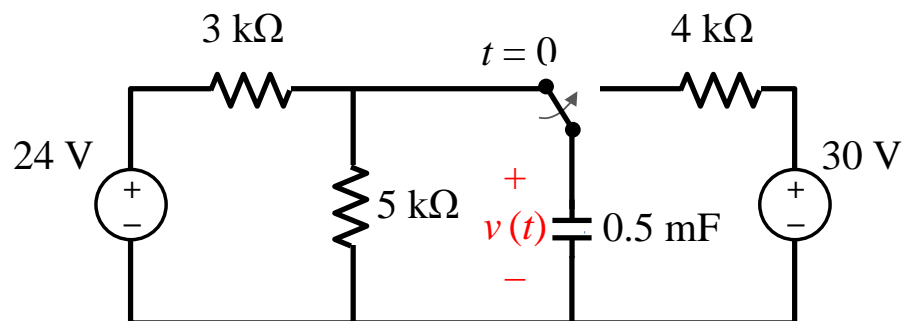
## Step response:

- When the state of the switch is changed, the new state has new sources
- The new sources cause new responses—**forced responses**
- If the new sources are DC inputs, then the force response is called the “**step response**”




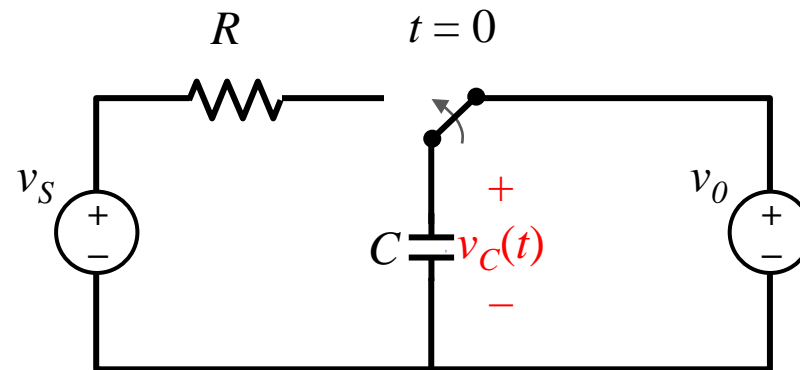


1. Find  $v_C(t)$  for  $t \geq 0^+$

## EX 3.11
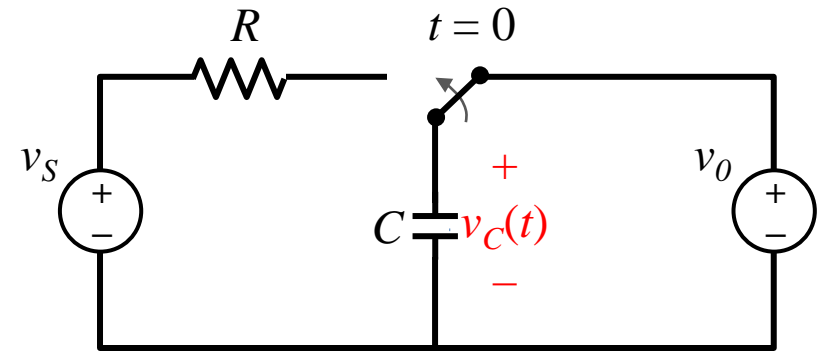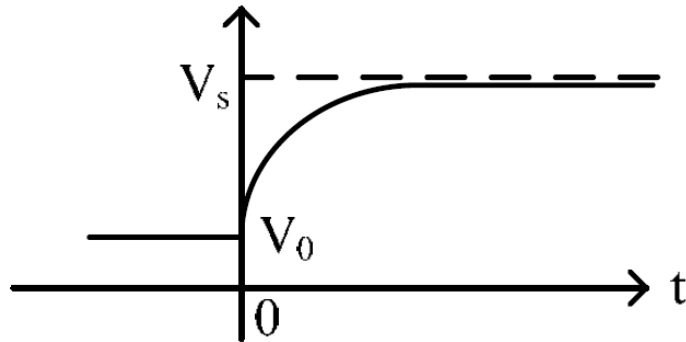
## Basic Case of Step Response (2/2)


The complete solution:  $v_C(t) = (V_0 - V_S)e^{-\frac{t}{RC}} + V_S$



How about the current over  $C$ ?

$$i_C(t) = C \frac{dv_C}{dt} = C \left[ \frac{-1}{RC} (v_0 - v_S) e^{-\frac{t}{RC}} \right] = \frac{v_S - v_0}{R} e^{-\frac{t}{RC}}$$

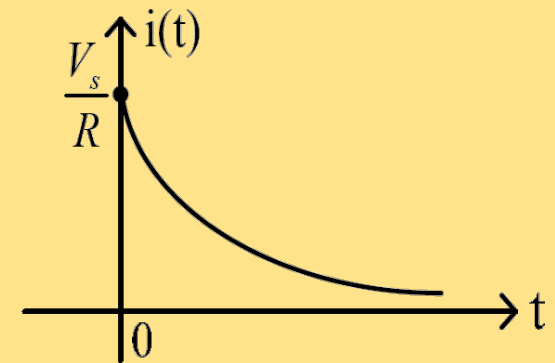If  $v_0 = 0$ , for  $t = 0^+$ ,  $i(0^+) = v_S/R$   
 $C$  is initially short circuited!





# Particular Solutions (1/2)

$$a_n y^{(n)}(x) + a_{n-1} y^{(n-1)}(x) + \cdots + a_1 y'(x) + a_0 y = g(x)$$

解的形式為  $y_h + y_p$  :

$g(x)$  長什麼樣子，particular solution 就是什麼樣子

1. 1 (any constant)	$A$
2. $5x + 7$	$Ax + B$
3. $3x^2 - 2$	$Ax^2 + Bx + C$
4. $x^3 - x + 1$	$Ax^3 + Bx^2 + Cx + E$
5. $\sin 4x$	$A \cos 4x + B \sin 4x$
6. $\cos 4x$	$A \cos 4x + B \sin 4x$
7. $e^{5x}$	$Ae^{5x}$
8. $(9x - 2)e^{5x}$	$(Ax + B)e^{5x}$
9. $x^2 e^{5x}$	$(Ax^2 + Bx + C)e^{5x}$
10. $e^{3x} \sin 4x$	$Ae^{3x} \cos 4x + Be^{3x} \sin 4x$
11. $5x^2 \sin 4x$	$(Ax^2 + Bx + C) \cos 4x + (Ex^2 + Fx + G) \sin 4x$
12. $xe^{3x} \cos 4x$	$(Ax + B)e^{3x} \cos 4x + (Cx + E)e^{3x} \sin 4x$





# Particular Solutions (2/2)

## Example

$$y'' - 2y' - 3y = \underline{4x - 5} + \underline{6xe^{2x}}$$

Step 1: Find the solution of

$$y'' - 2y' - 3y = 0.$$

$$y_c = c_1 e^{3x} + c_2 e^{-x}$$

Step 2: Particular solution

$$y'' - 2y' - 3y = 4x - 5$$

guess

$$y_{p_1} = Ax + B$$

$$y_{p_1} = -\frac{4}{3}x + \frac{23}{9}$$

$$y'' - 2y' - 3y = 6xe^{2x}$$


guess

$$y_{p_2} = Cxe^{2x} + Ee^{2x}$$

$$y_{p_2} = -(2x + \frac{4}{3})e^{2x}$$


## EX 3.12

# An RC Circuit with Step Responses

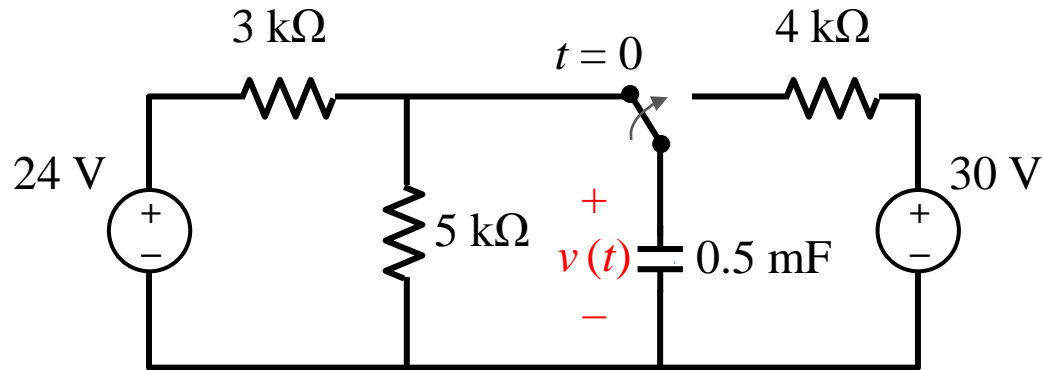

  $t \leq 0^-$  : the circuit is under steady state

1. Find  $v(t)$  for  $t \geq 0^+$

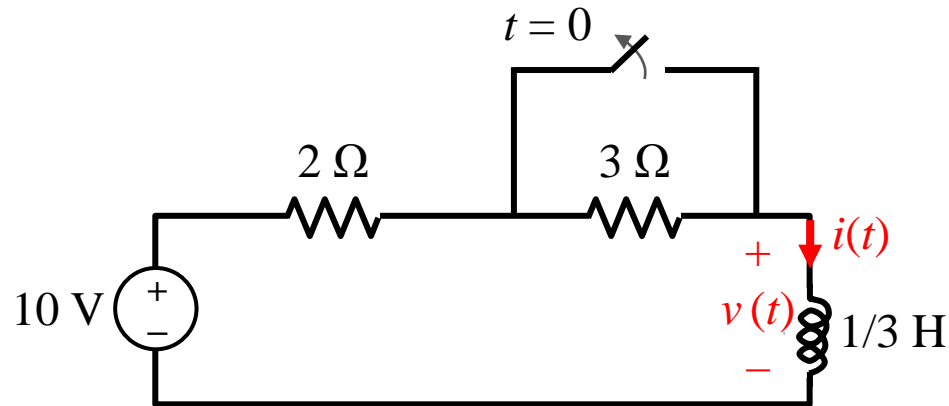



  $t \leq 0^-$  : the circuit is under steady state

1. Find  $v(t)$  for  $t \geq 0^+$
2. Find  $i(t)$  for  $t \geq 0^+$

## EX 3.14

## First-Order RC Circuit

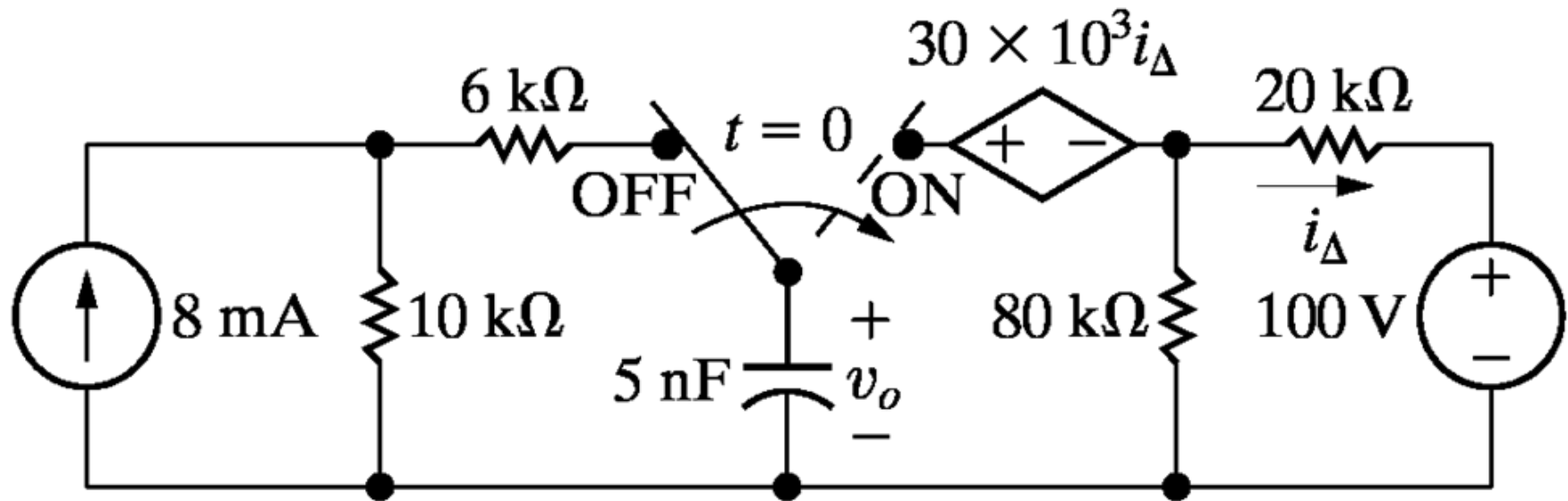


 The switch in the circuit has been in the OFF position for a long time

1. Find  $v_o(t)$  for  $t \geq 0^+$
2. Find  $i_\Delta(t)$  for  $t \geq 0^+$

## EX 3.15

## First-Order RL Circuit

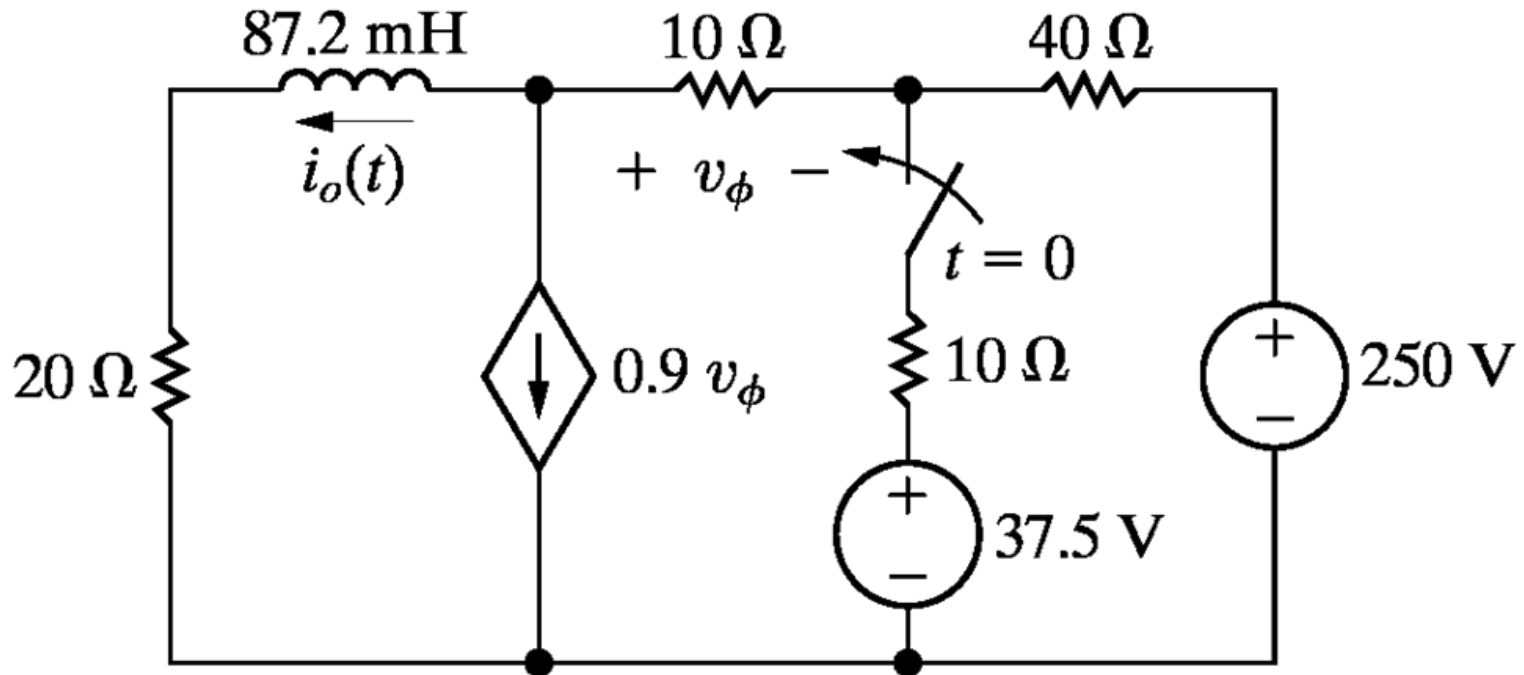


 The switch in the circuit has been open a long time before closing at  $t = 0$

1. Find  $i_o(t)$  for  $t \geq 0^+$

## EX 3.16

## First-Order RL Circuit

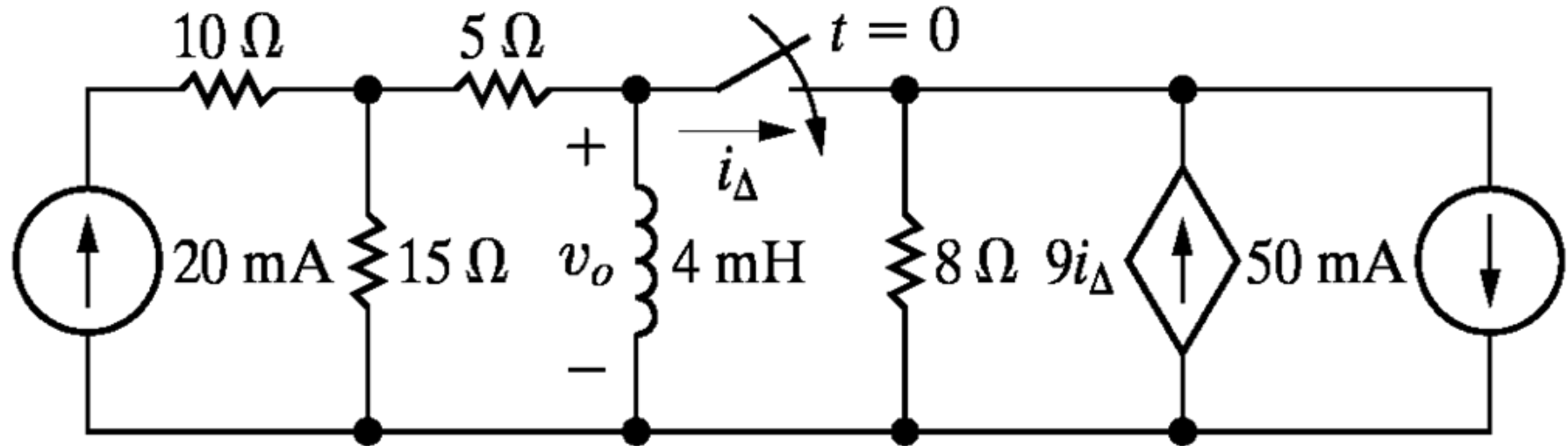

The switch in the circuit has been open a long time before closing at  $t = 0$

1. Find  $v_o(t)$  for  $t \geq 0^+$



# Contents



## **3.5 Linear Second-Order Circuits**






# Examples of Linear 2<sup>nd</sup>-Order Circuits (1/2)


- One energy storage element
- 1<sup>st</sup>-order differential equations
- Need one initial condition to get the unique solution

- Two energy storage elements
- 2<sup>nd</sup>-order differential equations
- Need two initial conditions to get the unique solution

Series RLC Circuit


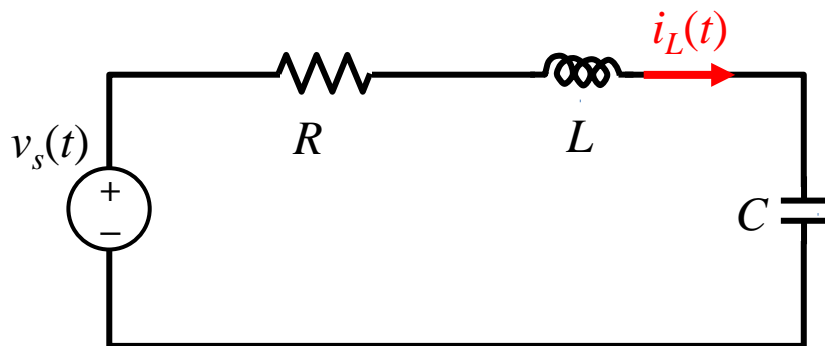



Parallel RLC Circuit

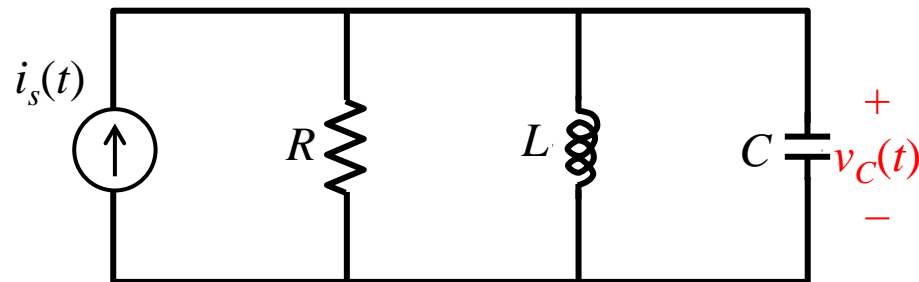


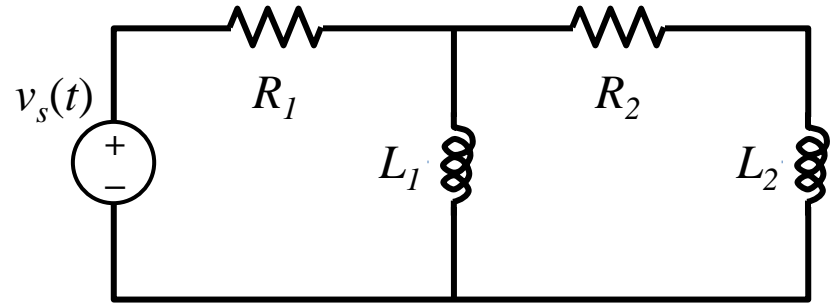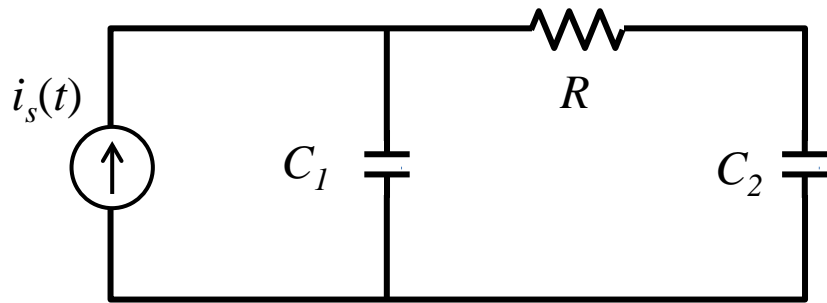
## Examples of Linear 2<sup>nd</sup>-Order Circuits (2/2)




 We can't combine  $C_1$  and  $C_2$  ( $L_1$  and  $L_2$ ) together because there is a resistor between them




# Examples of Natural Response

## Series RLC Circuit

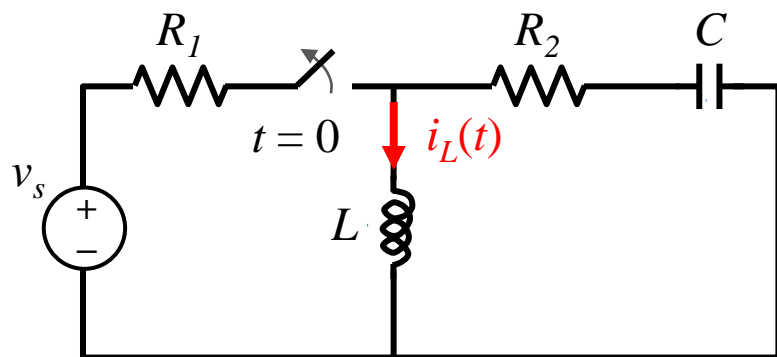

## Parallel RLC Circuit

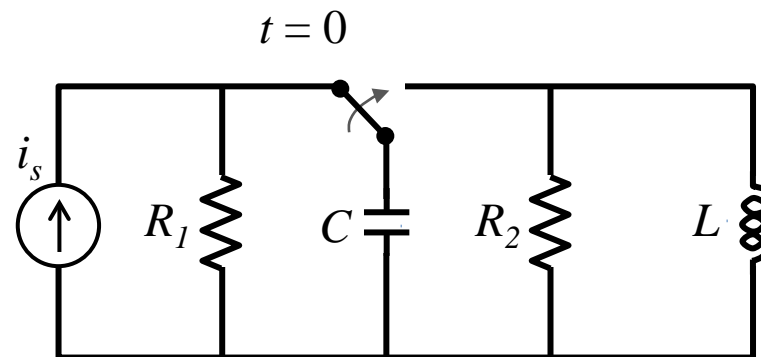


- When the switch is turned off, the new circuit has no external sources




# Examples of Step Response

## Series RLC Circuit

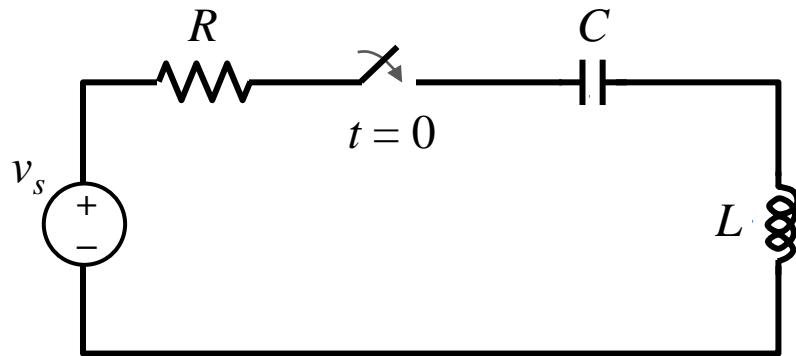


## Parallel RLC Circuit

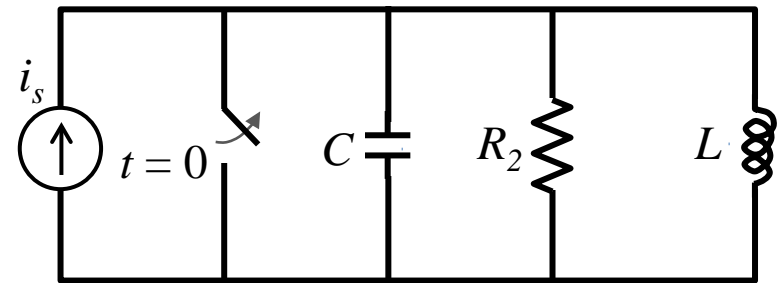

When the switch is turned off, the new circuit has external sources


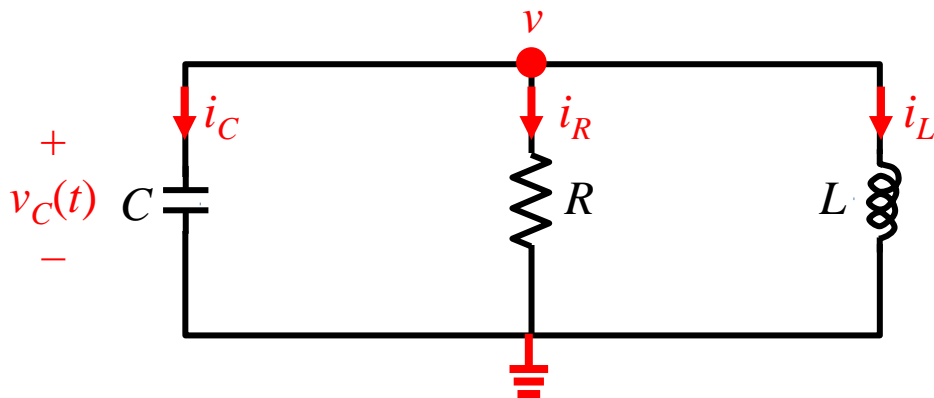
# How to Solve 2<sup>nd</sup>-Order RLC Circuits? (1/4)



Objective: find  $v_C(t)$

1. Select the nodal analysis or mesh analysis and write down the equation

$$\left( C \frac{dv(t)}{dt} \right) + \left( \frac{v(t)}{R} \right) + \left( \frac{1}{L} \int_{0^+}^t v d\tau + i(0^+) \right) = 0$$

2. Differentiate the equation as many times as required to get the standard form of a 2<sup>nd</sup>-order differential equation

$$C \frac{d^2 v(t)}{dt^2} + \frac{1}{R} \frac{dv(t)}{dt} + \frac{1}{L} v(t) = 0$$



# How to Solve 2<sup>nd</sup>-Order RLC Circuits? (2/4)

3. Solve the differential equation

- ① Homogeneous solutions  $v_h(t)$
- ② Particular solution  $v_p(t)$  (if the RLC circuit has external sources)

$$C \frac{d^2 v(t)}{dt^2} + \frac{1}{R} \frac{dv(t)}{dt} + \frac{1}{L} v(t) = 0$$

Considering that the RLC circuit has no external sources (as this example):

- ① Homogeneous solutions  $x_h(t)$ :

Suppose that the solutions have the form of  $e^{mt}$

$$Cm^2 e^{mt} + \frac{m}{R} e^{mt} + \frac{1}{L} e^{mt} = 0 \rightarrow \left( Cm^2 + \frac{m}{R} + \frac{1}{L} \right) e^{mt} = 0$$



# How to Solve 2<sup>nd</sup>-Order RLC Circuits? (3/4)

$$\text{Solving } Cm^2 + \frac{m}{R} + \frac{1}{L} = 0:$$

$$\begin{aligned} \rightarrow m_1 &= -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \\ m_2 &= -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \end{aligned}$$





First difference between 1<sup>st</sup>-order and 2<sup>nd</sup>-order circuits

$$\sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} > 0, < 0, \text{ or } = 0 \text{ leads to three different situations}$$

- Three new terminologies: overdamped, underdamped, & critically damped


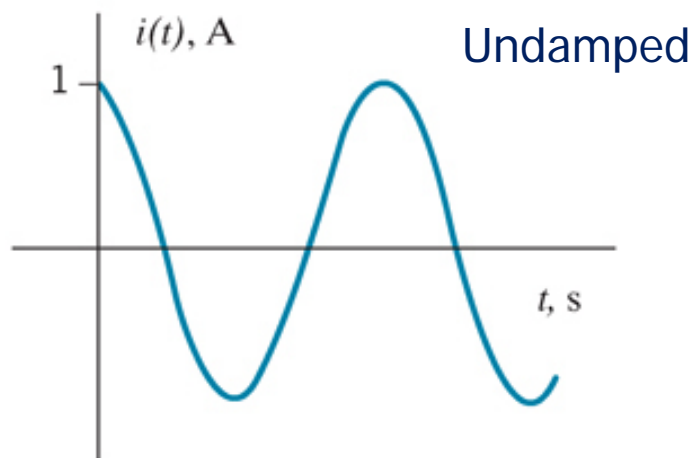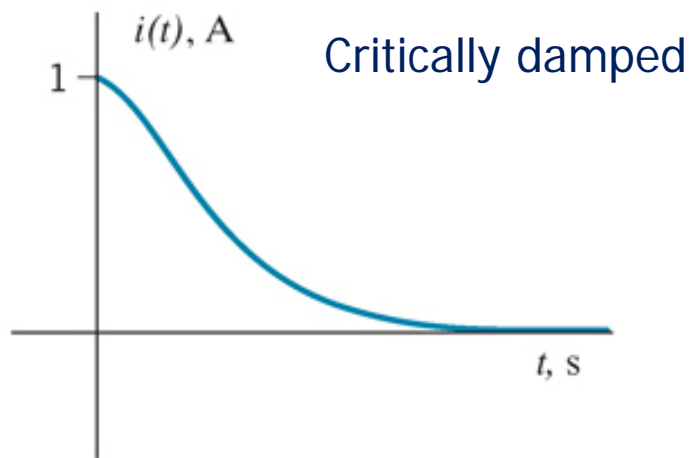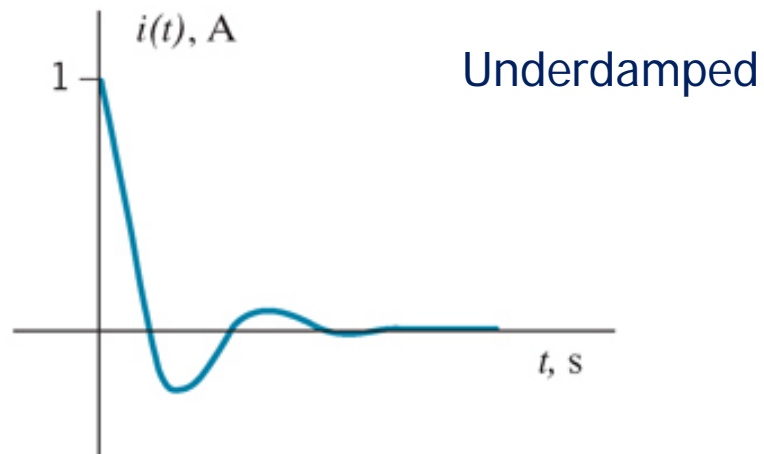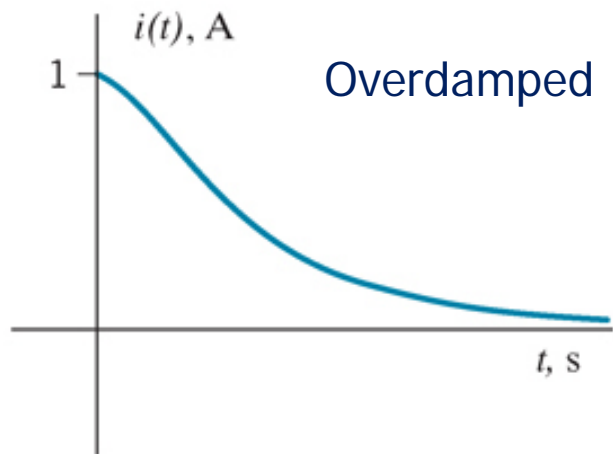
# Overdamped, Underdamped, & Critically damped







# How to Solve 2<sup>nd</sup>-Order RLC Circuits? (4/4)

4. Express the final solution  $v(t) = v_h(t) + v_p(t)$

(Supposing  $\sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} > 0$ )

➔  $v_C(t) = c_1 e^{m_1 t} + c_2 e^{m_2 t}$

## Second difference between 1<sup>st</sup>-order and 2<sup>nd</sup>-order circuits

- In order to get the unique solution, we need to solve  $c_1$  and  $c_2$
- Two initial conditions (I. C.) are required (Lectures 3-2 and 3-3 only need one I. C.)
- What I. C. do we need?

$$v_C(0^+), \frac{dv_C(0^+)}{dt}$$



# Contents



## **3.6 Responses of Second-Order Circuits**



# Solution Procedure

All the problems in these two lectures can be casted into:

Step 1: ■ Draw the circuit under  $t \leq 0^-$

■ Find  $i_L(0^-)$  on the inductor and  $v_C(0^-)$  on the capacitor

Step 2: ■ Draw the circuit for  $t \geq 0^+$


■ Formulate the problem by nodal analysis or mesh analysis


■ Differentiate the equation as many times as required to get the standard form of a 2<sup>nd</sup> order D. E.

$$a \frac{d^2 x(t)}{dt^2} + b \frac{dx(t)}{dt} + x(t) = y(t)$$

Step 3: ■ Solve the D. E. to get  $x(t) = x_h(t) + x_p(t)$

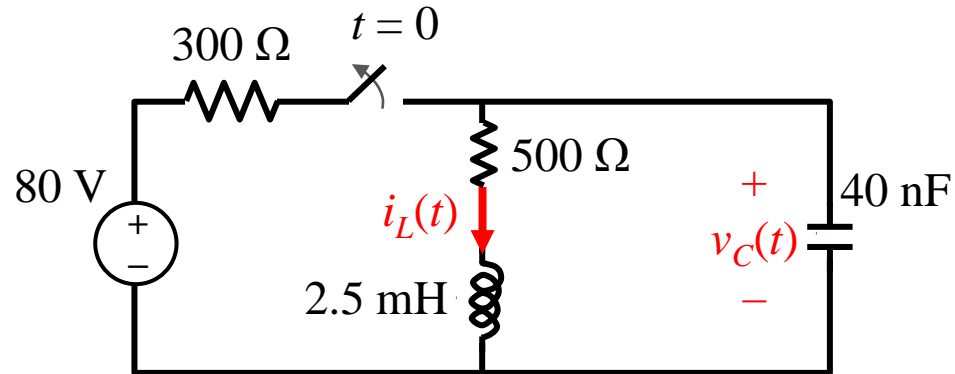■ Find the initial conditions  $x(0^+)$  and  $dx(0^+)/dt$  and then get the unique solution





  $t \leq 0^-$ : the circuit is under steady state

1. Find  $i_L(t)$  for  $t \geq 0^+$


# EX 3.18
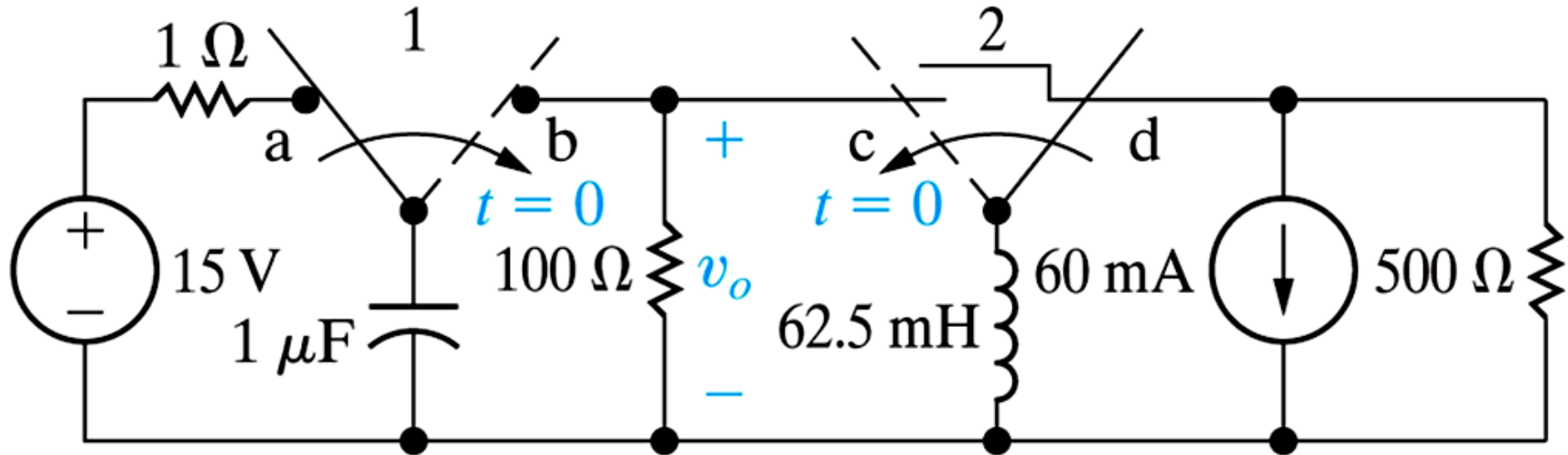
## Natural Response of Parallel RLC Circuits




  $t \leq 0^-$ : the circuit is under steady state

1. Find  $v_o(t)$  for  $t \geq 0^+$

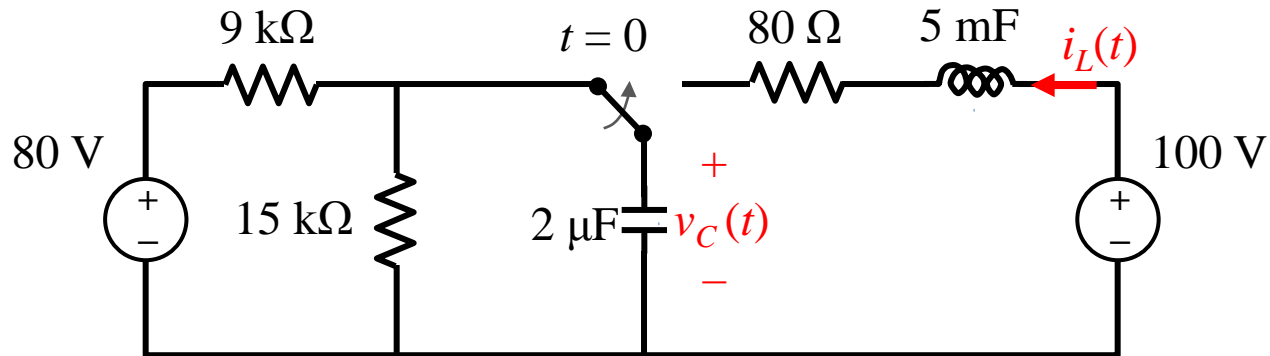

  $t \leq 0^-$ : the circuit is under steady state

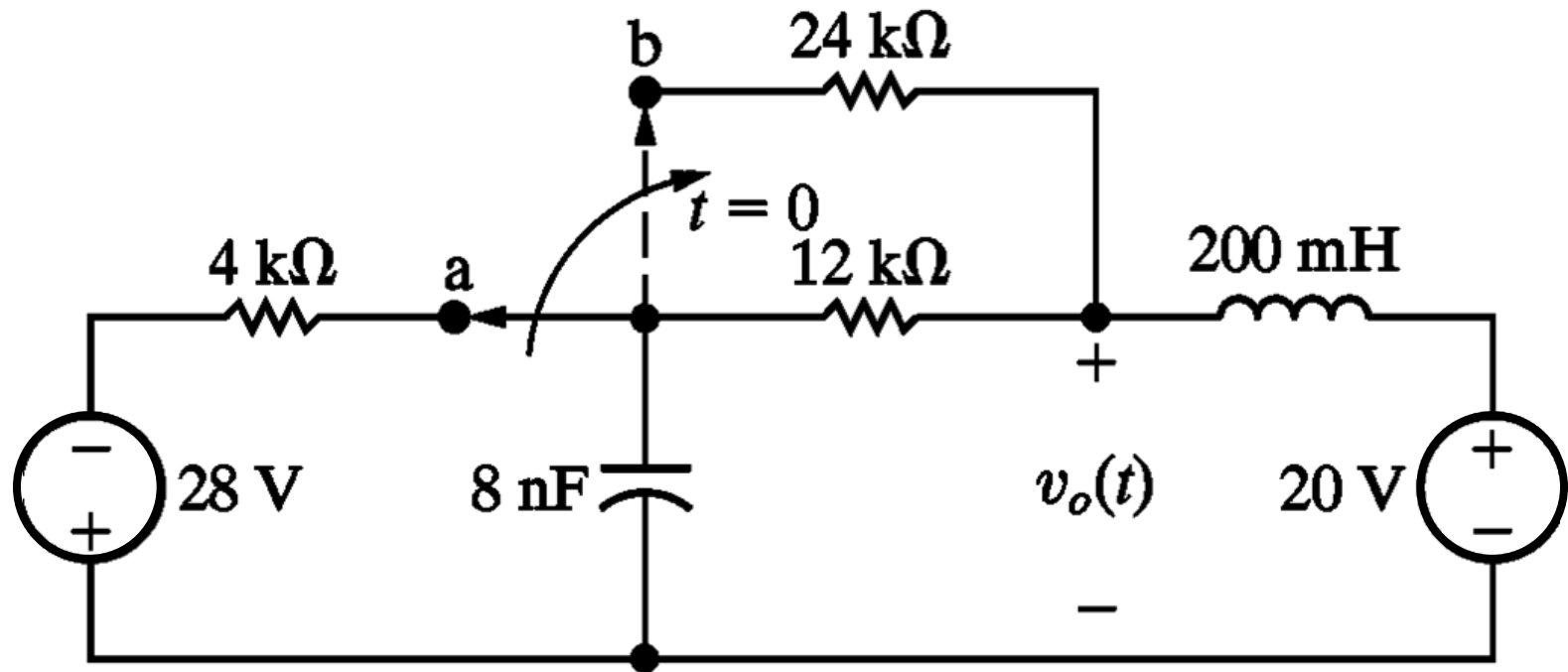1. Find  $i_L(0^+)$  for  $t \geq 0^+$
2. Find  $di_L(0^+)/dt$  for  $t \geq 0^+$
3. Find  $i_L(t)$  for  $t \geq 0^+$





■ The switch in the circuit has been in position  $a$  for a long time

1. Find  $i_L(t)$  for  $t \geq 0^+$

## EX 3.21

## A More Complex Example

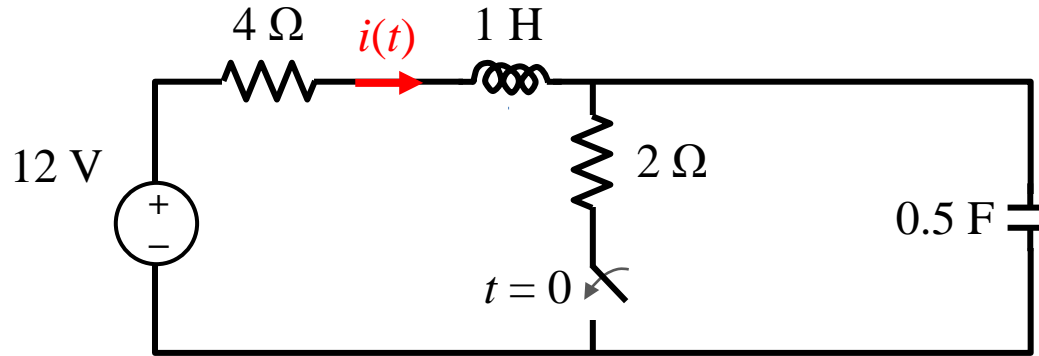

  $t \leq 0^-$ : the circuit is under steady state

1. Find  $i(0^+)$  for  $t \geq 0^+$
2. Find  $di(0^+)/dt$  for  $t \geq 0^+$
3. Find  $i(t)$  for  $t \geq 0^+$