

數位邏輯設計 Ch2 HW

注意事項：請寫出詳細計算與分析過程，不可以只寫答案！

Problems:

- 2.1 Draw the symbol for the NOT gate (inverter) in both rectangular-outline and distinctive-shape forms.
- 2.5 Write a sentence that describes the operation of a 4-input OR gate with inputs J , K , L , and M and output N . Make the truth table of this gate and draw an asterisk beside the line(s) of the truth table indicating when the gate output is in its active state.
- 2.7 State how four switches must be connected to represent a 4-input OR function. Draw a circuit diagram showing how this function can control a lamp.
- 2.15 A pump motor in an industrial plant will start only if the temperature and pressure of liquid in a tank exceed a certain level. The temperature sensor and pressure sensor, shown in Figure 2.47 each produce a logic HIGH if the measured quantities exceed this value. The logic circuit interface produces a HIGH output to turn on the motor. Draw the symbol and truth table of the gate that corresponds to the action of the logic circuit.

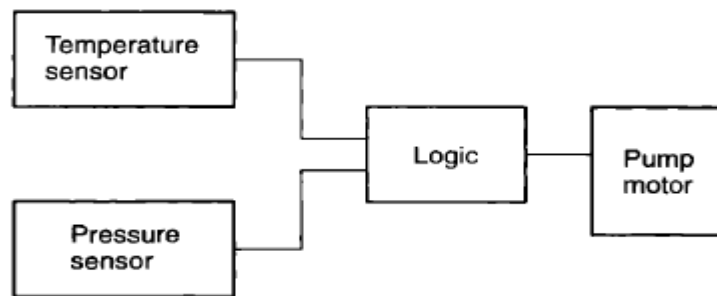


FIGURE 2.47 Problem 2.15: Temperature and Pressure Sensors

- 2.25 Refer to Figure 2.51. State which two gates of the three shown are DeMorgan equivalents of each other. Explain your choice.

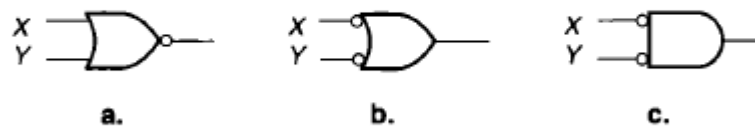


FIGURE 2.51 Problem 2.25: Logic Gates

- 2.35 The A and B waveforms shown in Figure 2.53 are inputs to an OR gate. Complete the sketch by drawing the waveform for output Y .

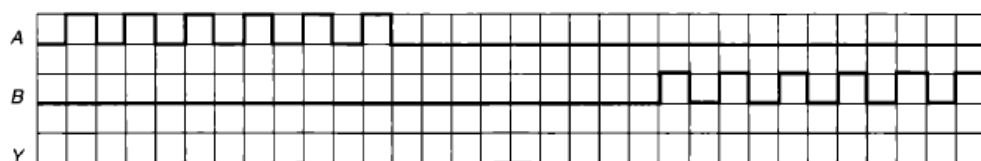


FIGURE 2.53 Problem 2.35: Waveforms