
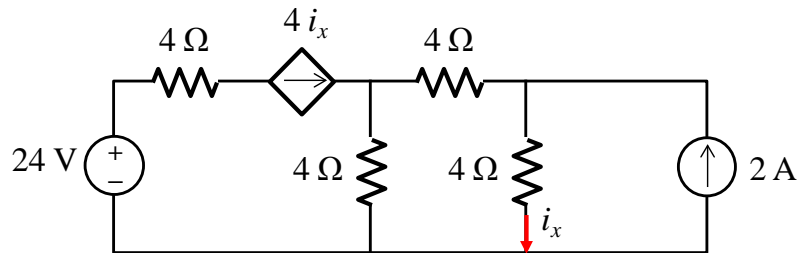


**Name:**

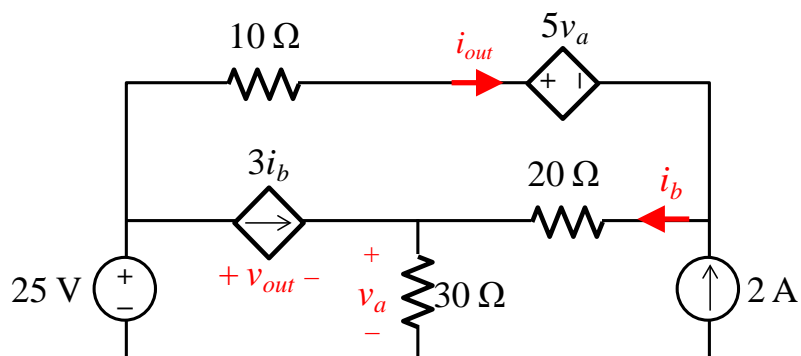
1. Considering the following circuit,
  - (a) (10%) calculate the power of the current-controlled current source;
  - (b) (10%) calculate the power of the independent current source.




2. Considering the following circuit,
  - (a) (10%) find the output voltage  $v_{out}$ ;
  - (b) (10%) calculate the power of the  $5v_a$  dependent voltage source.



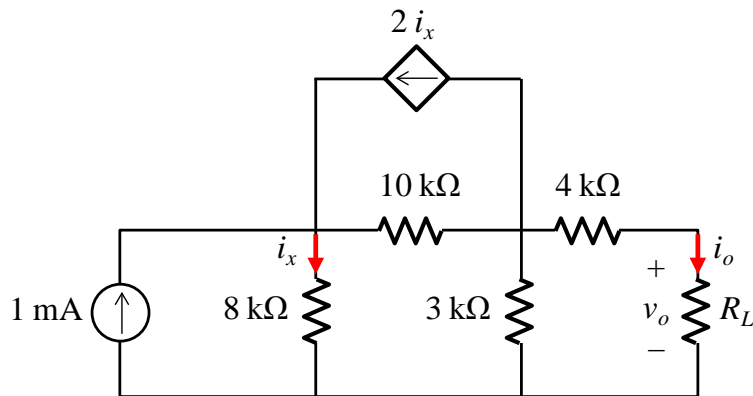3. A load with a resistance of  $R_L$  is connected to the circuit.
- (10%) Find the output voltage  $v_o$  when  $R_L = 20\text{ k}\Omega$ ;
  - (10%) find the load resistance so that the output current  $i_o = 100\text{ mA}$ ;
  - (10%) find the power of the load when  $R_L = 10\text{ k}\Omega$ ;
  - (10%) find the load resistance so that the output power of the load is  $80\text{ mW}$ .



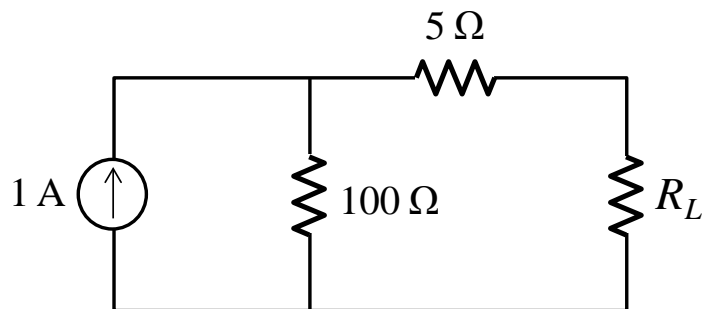4. A load with a resistance of  $R_L$  is connected to the circuit.
- (10%) Find the value of the variable resistor  $R_L$  that will result in maximum power transfer to the load.
  - (10%) When  $R_L$  is adjusted for maximum power transfer, what percentage of the power delivered by the 1-A source reaches  $R_L$ ?



**Please detail the computational process. Failure to do so will result in less or no points at all.**